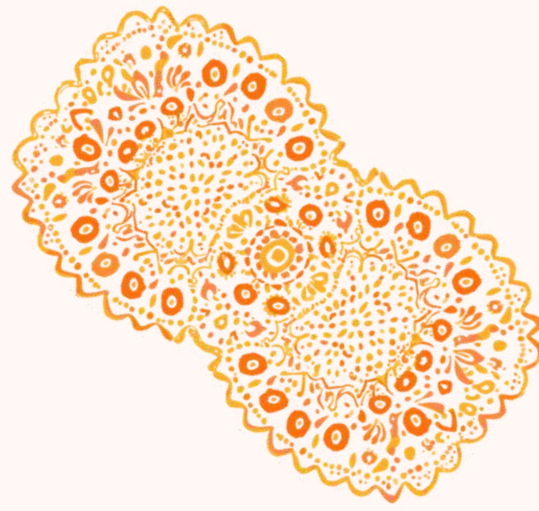




LED DICE — RANDOM NUMBER!




Build • Play • Learn

Let's Roll!



The Story of the Missing Dice

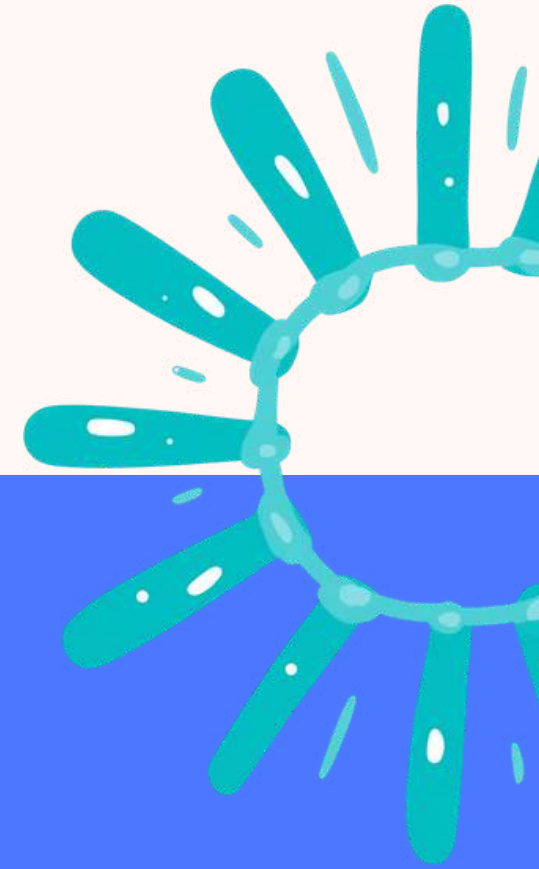

What if we lose our dice while playing Ludo? How can we play now? Let's build our own LED Dice!



What is a Random Number?



A surprise number we cannot guess!
Like picking a name from a hat — we don't know who it will be! In India, we play "Chit-picking" games where we fold paper slips and pick one without looking. That's random!



Meet the Circuit Parts


Battery — Power source!

Push-button Switch — Input!

LED Light — Output glow!



Input vs Output

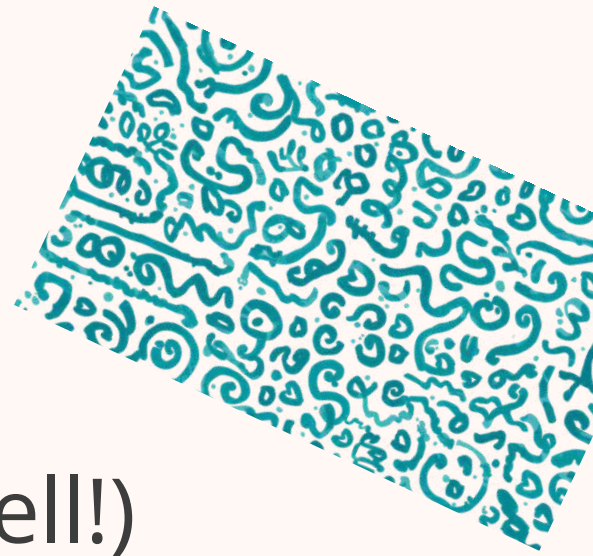

Input: Press the button (like ringing a doorbell!)

Output: LED glows (like the doorbell sound!)

Button = Input, LED = Output!



The Circuit Loop — How Electricity Flows



Electricity needs a complete circle called "Circumambulation"! If the path breaks anywhere, no power flows. Think of it like walking around a temple — you must complete the full circle, you cannot stop halfway! Our LED Dice works the same way.





What's Inside Your LED Dice Kit?

Your kit has everything you need!

- Pre-stripped wires
- Coin-cell battery
- Colorful housing
- Push-button switch
- LED lights

No scissors needed — safe and ready to build!




How Does the Button Talk to the LED?

Press the button → Electricity flows → LED glows! When you push the button, it completes the circuit loop. The electricity travels from the battery through the wire to the LED. The LED lights up like a Jugnu (firefly)!




Let's Build the LED Dice! (Step 1)

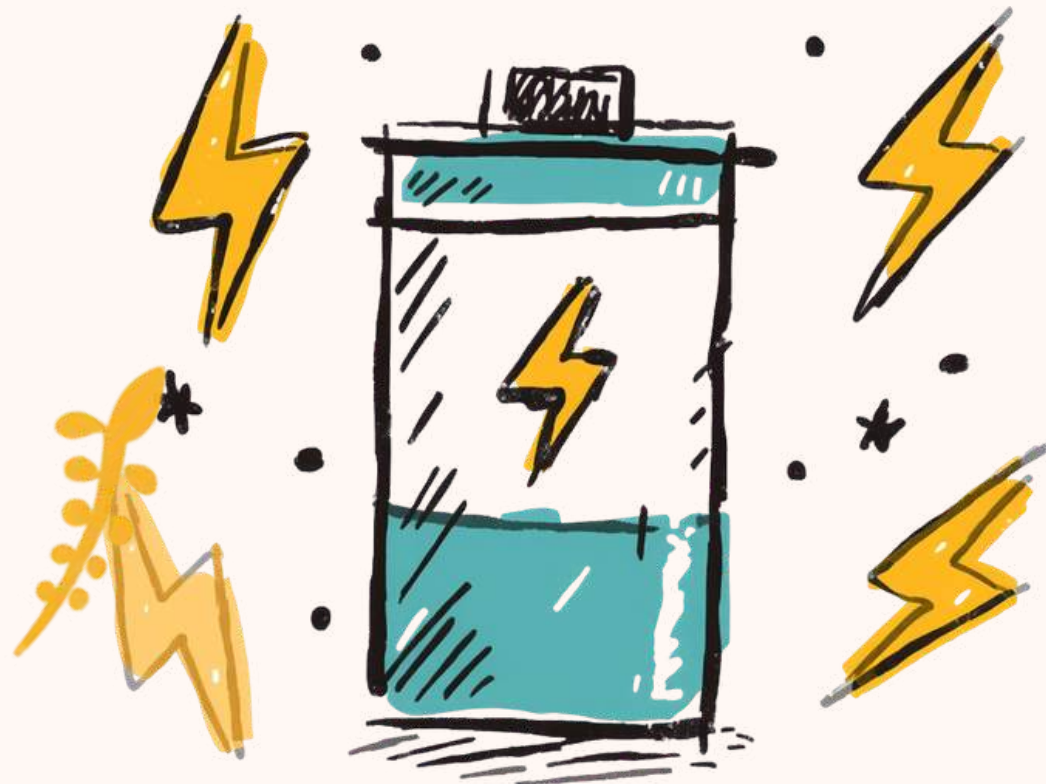Connect battery to wire!
This is easy-peasy! No grown-ups needed. Just click the wire onto the battery. You're becoming a circuit builder!





Let's Build the LED Dice! (Step 2)

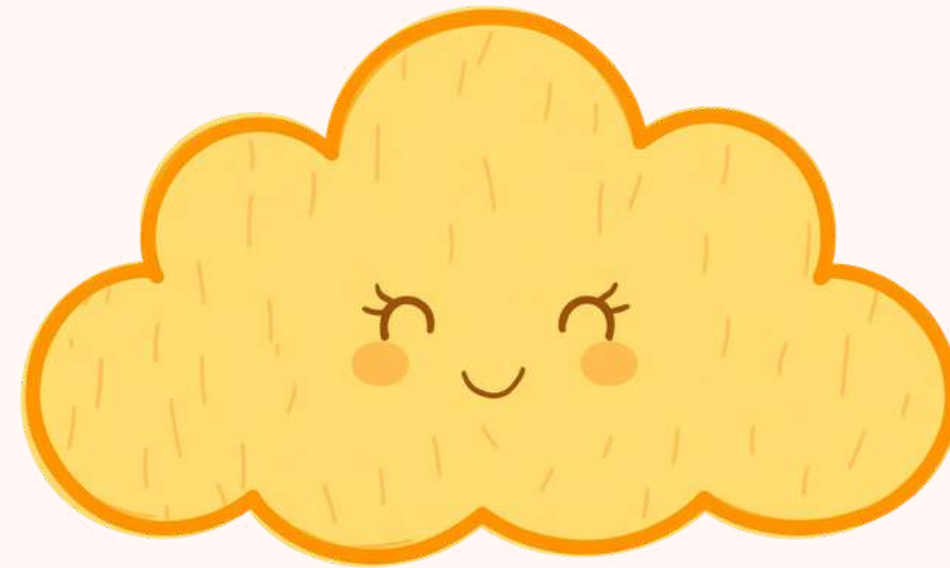
Attach switch to circuit — Click the switch part in place! It's easy, beta!



Let's Build the LED Dice! (Step 3)

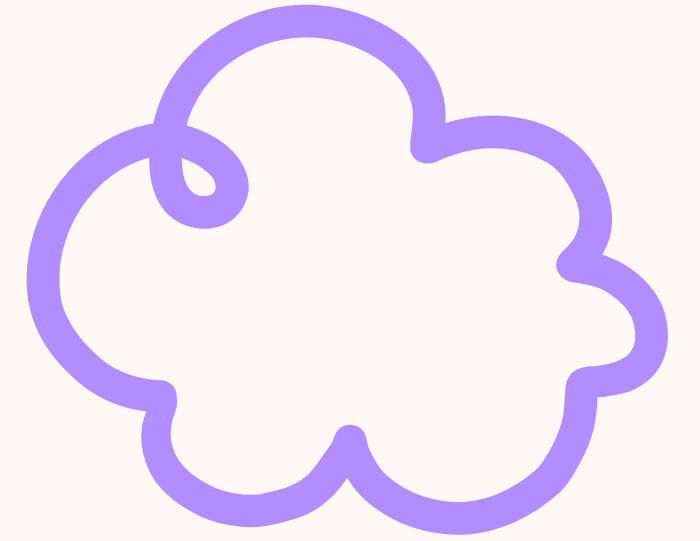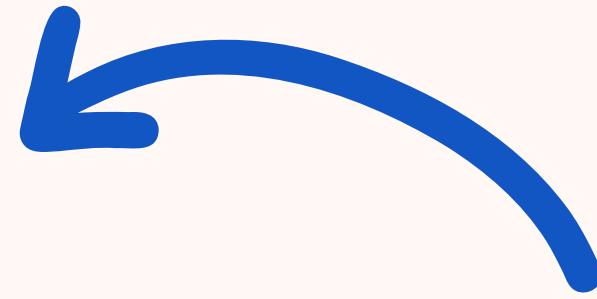

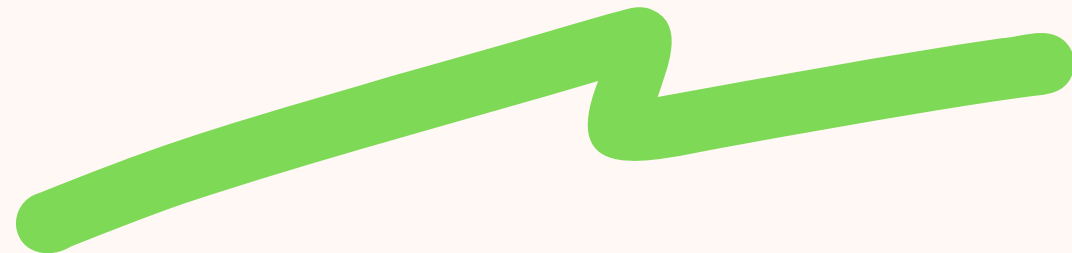
Connect LED light to finish circuit!
Press the button, beta! See the Jugnu glow!
Your LED Dice is ready to play!





Game Time! Play Ludo with Your LED Dice

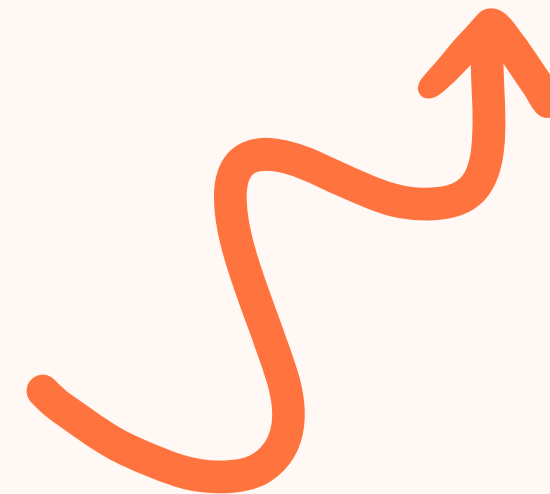Roll your LED dice to move your token! Play a quick 5-step race with friends. Press the button, see the number glow, and take your turn!



Safety First!



- Use only kit parts — no extra items!
- No scissors or sharp tools needed
- Handle the battery gently
- Ask a grown-up if you feel unsure
- Keep small parts away from mouth



What Did We Learn Today?



- ✨ Random number means surprise!
- 🔄 Circuits need a complete loop
- 👉 Button = Input, LED = Output
- 🎲 We built our own LED Dice!
- 🌟 Science is fun and everywhere!



Keep Creating with resourceful solution”!

Be a creative problem-solver every day!
Remember, science is everywhere around you. Keep exploring, keep building, and never stop asking questions!

Thank you for learning with us! 🌟

