




# COPPER TAPE LIGHTHOUSE

Light Up Your Lighthouse! STEM & Electronics


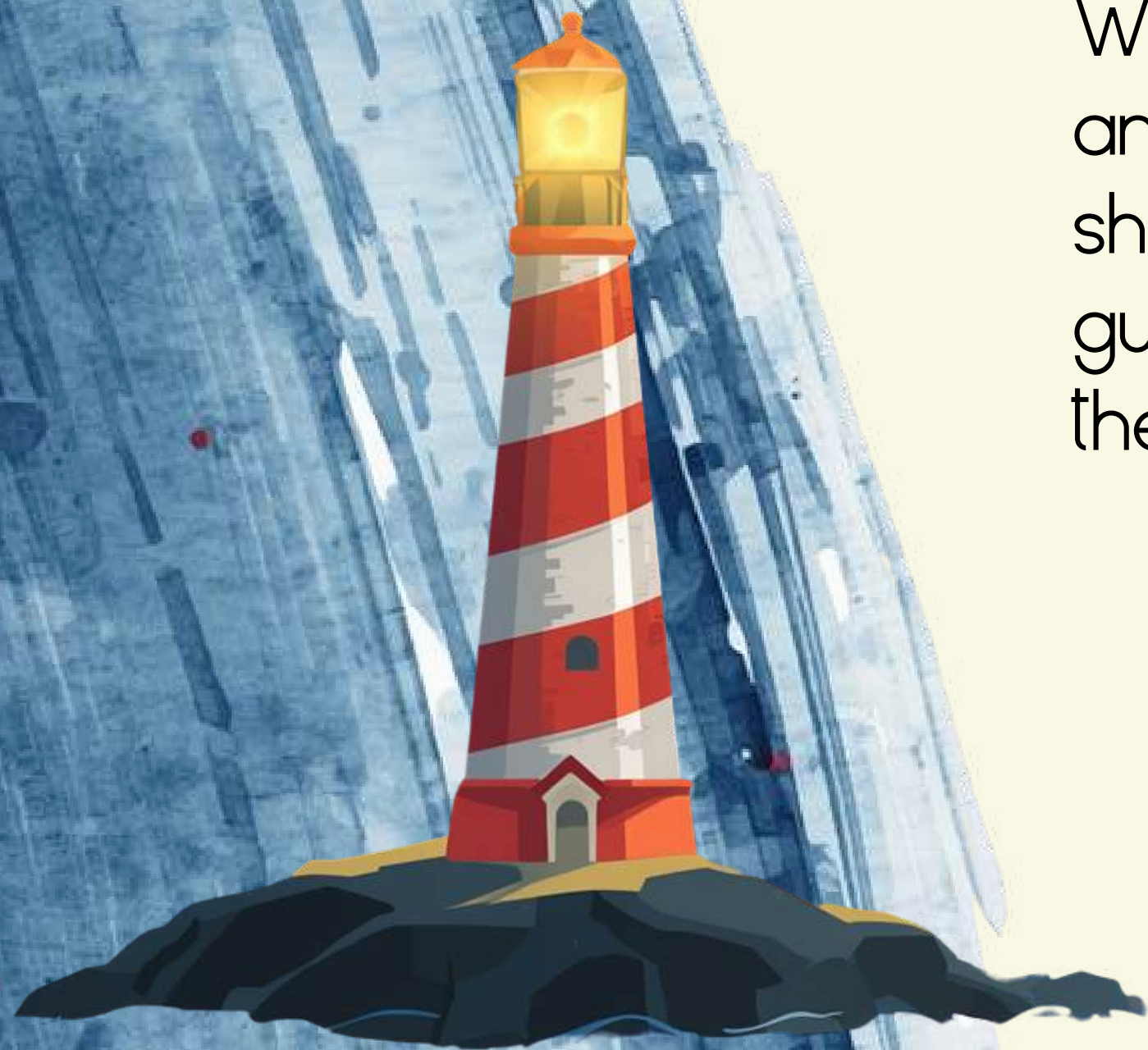
# THE STORY OF THE SEA

Why do ships need lights at night? The sea is dark and dangerous! Lighthouses, called "Lighthouse help ships find their way safely home. Indian coastal guards use these tall towers to guide boats through the "Path of electricity" - the path of light!



# MEET THE TOOLS

Our Circuit Friends:


- LED - "Small Light" (tiny lamp)
- Coin Cell Battery - "Power Button"
- Copper Tape - "Shiny Tracks"




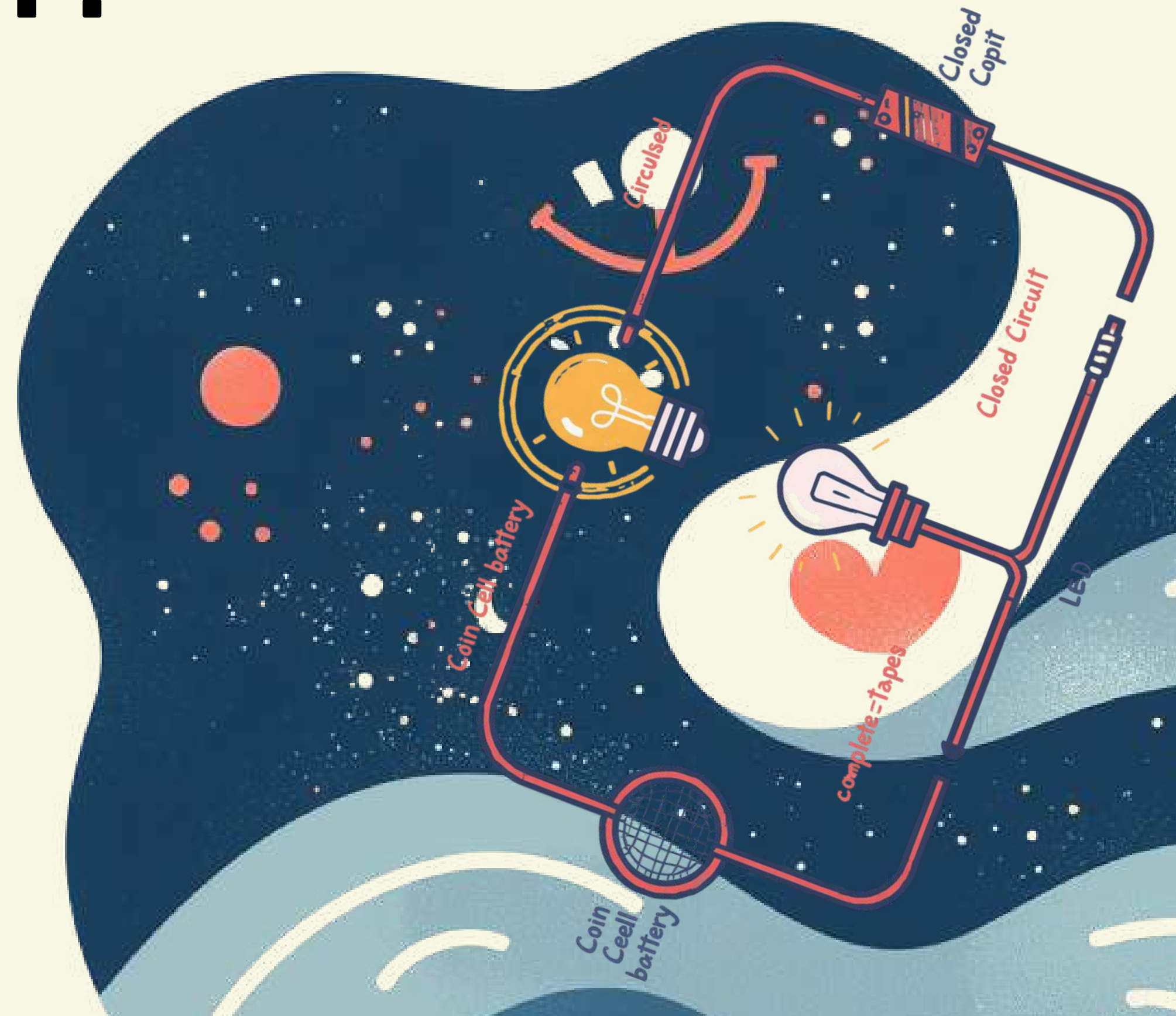
# WHAT IS A CIRCUIT?

Electricity flows like water in a pipe! A circuit is a "Waste paper" (path) that must be "Bandh" (closed) for to flow. Think of it as a loop - the electricity travels from the battery, through the shiny copper tape, lights up the LED, and comes back!



# INDIAN LIGHTHOUSES TO KNOW

Discover India's amazing lighthouses:

- Dolphin's Nose Lighthouse, Visakhapatnam
- Aguada Lighthouse, Goa
- Red-and-white striped lighthouses of Gujarat & Kerala



# BUILDING THE TRACK

Step 1: Peel and stick your copper tape along the dotted lines on your lighthouse template


Step 2: Press firmly to make a continuous "Shiny Track" with no gaps or breaks

Step 3: Keep your path closed - the tape must connect all the way around!


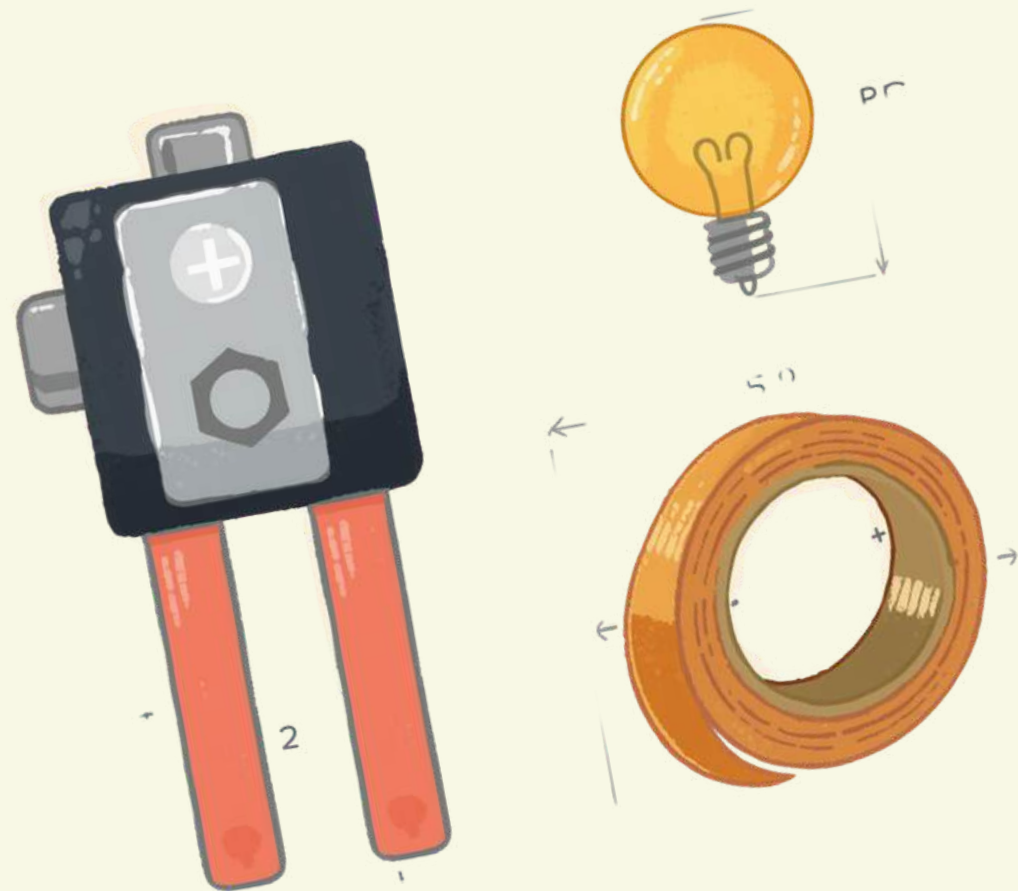
# PLACING BATTERY AND LED

Now complete your circuit! Place the coin cell battery flat on the copper tape with the positive (+) side up. Put your LED legs on the shiny tracks - long leg on positive, short leg on negative. You're the Electricity Detective!





# THE LIGHT-UP MOMENT!

Press down gently and watch the magic happen - Chamatkar! When your LED glows bright, you've completed the circuit! Celebrate your success - you made electricity flow through your very own lighthouse!





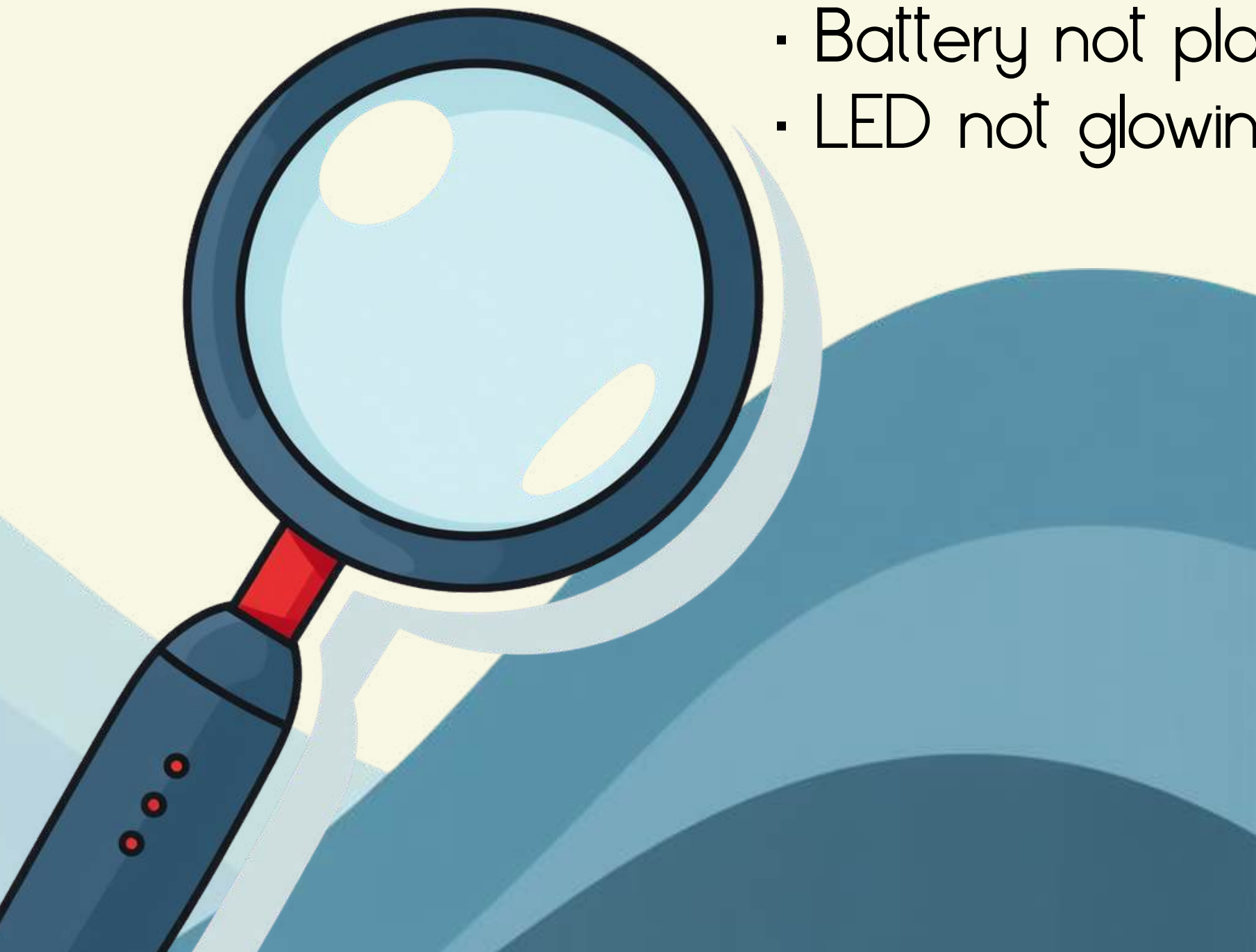
# DETECTIVE CHALLENGE

Check your "Path of electricity":

- Gaps in copper tape? Make the track continuous!
- Battery not placed correctly? Check the flat side!
- LED not glowing? Flip it around!



# DECORATION TIME!

Now make your lighthouse special! Add colors, stickers, waves, and ships. Draw the sea around it or add sparkly stars in the sky. This is YOUR lighthouse - let your creativity shine bright!



# SESSION RECAP & SUCCESS CRITERIA

Identify battery, copper tape, and LED  
Understand electricity needs a  
complete loop

Successfully light up the lighthouse LED

Name one Indian city with a lighthouse

You are now a Circuit Champion!





# THANK YOU!

Thank you for lighting up your lighthouse!  
Share your favorite part of the session  
Ask any questions you have  
Keep exploring STEM & Electronics!

