

LED CIRCUIT — MAKE A BUZZER BEEP!








**Aarav and Dada-ji need a
calling bell!
How to know when
someone comes?
Let's build a watchman
with light and sound!**



What is a Circuit?

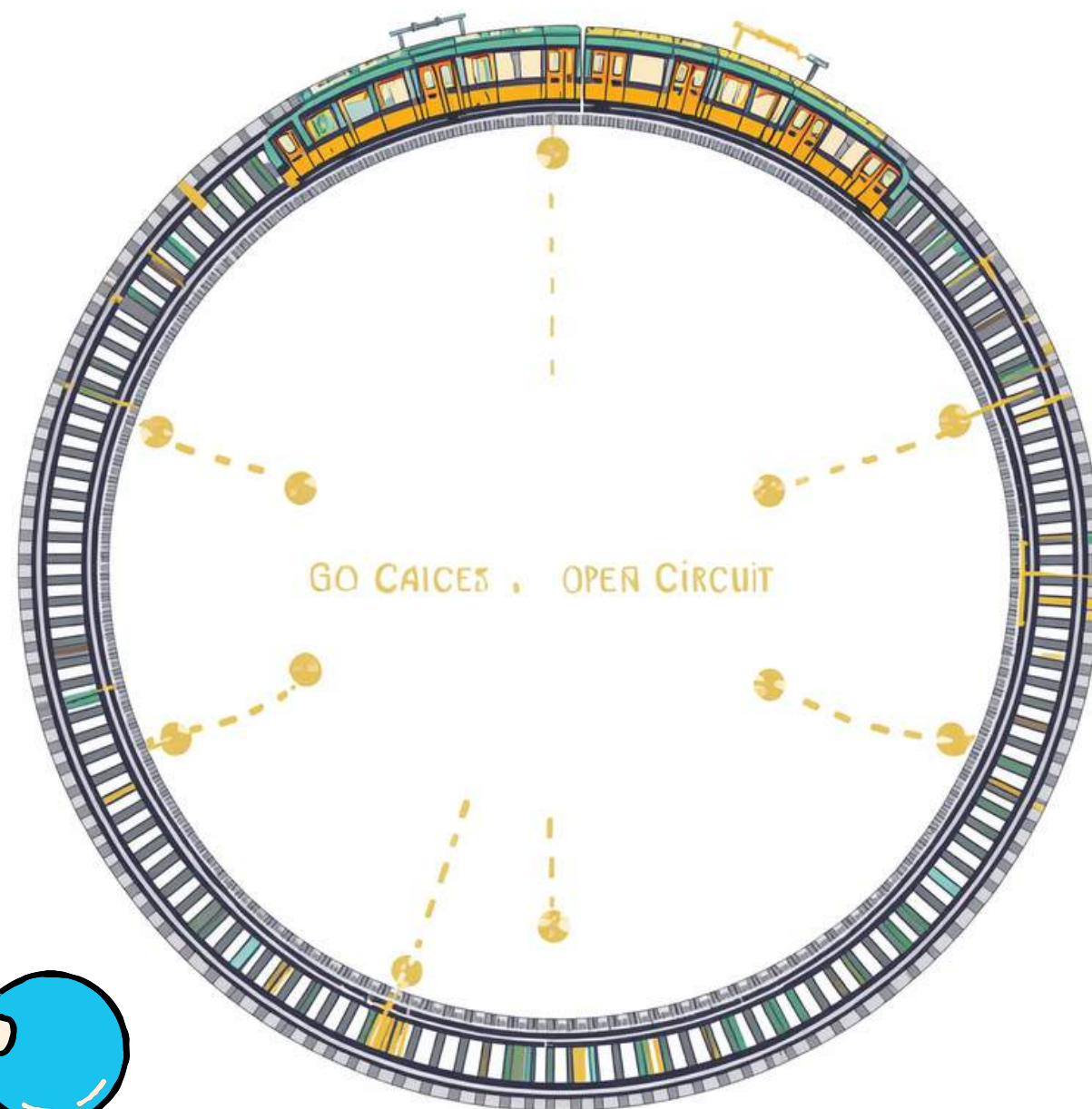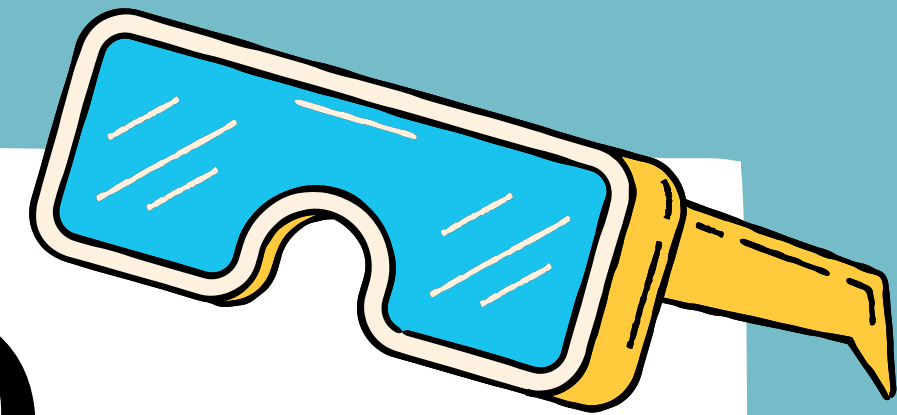

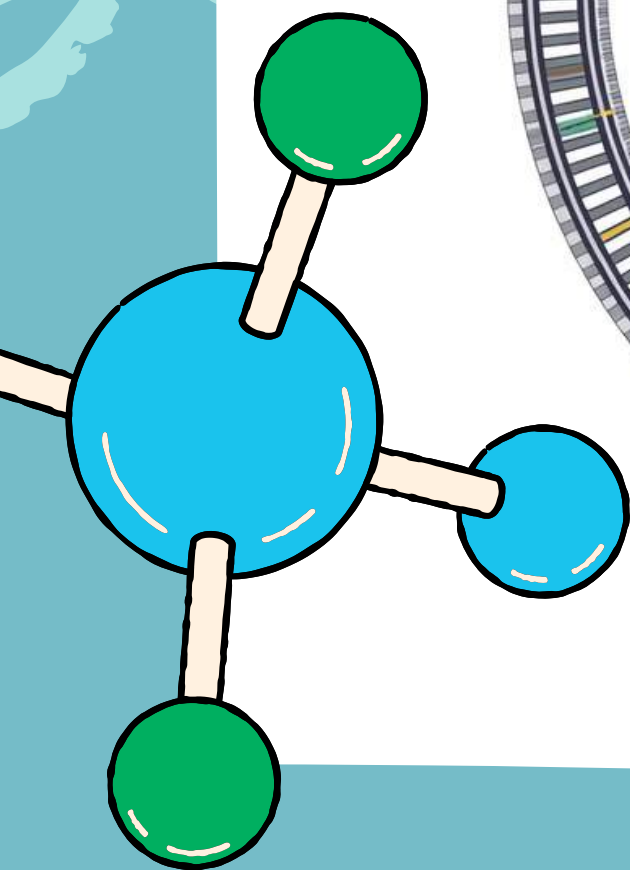A circuit is a
circle for
electricity to flow.
Like Delhi Metro
loop — if a bridge
breaks, no trains!



Battery — The Power Source

The Battery

Battery pushes electricity through the circuit. Just like a water tank pushes water through pipes!




Water Tank


Which side is positive?
The long leg of LED connects to the + side of the battery!




LED — The Festival Light!

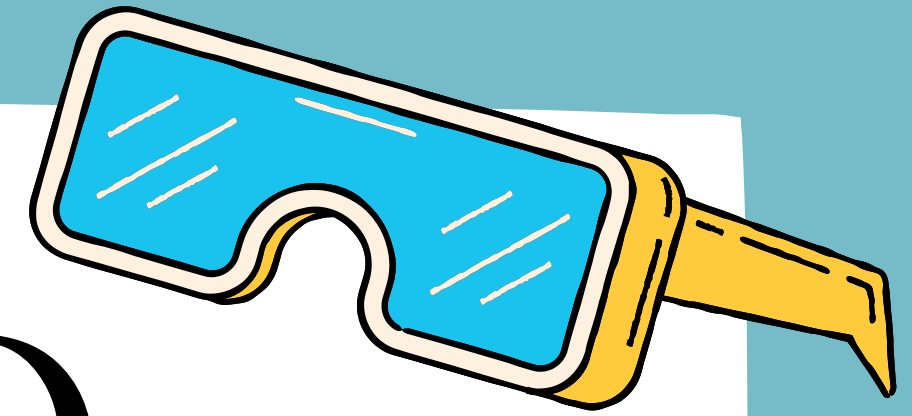

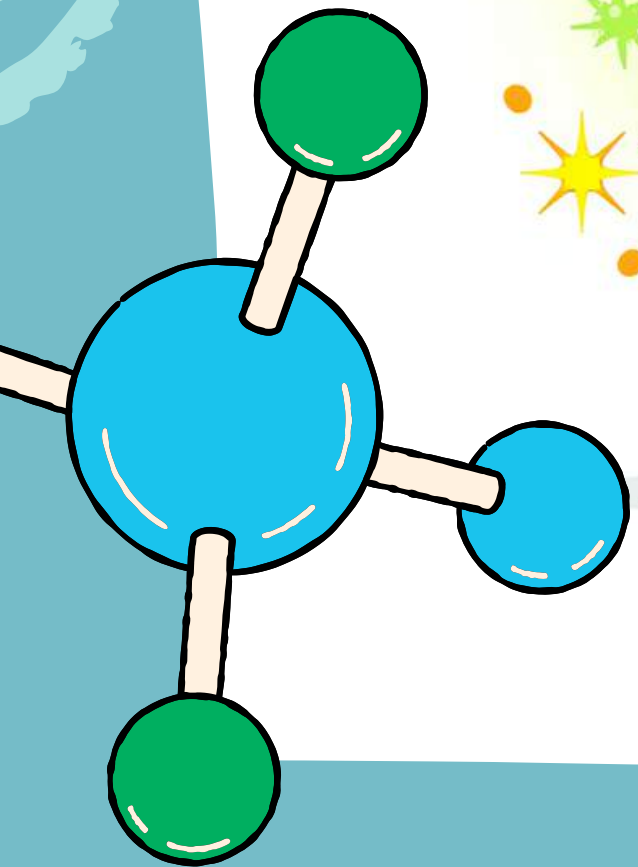
LED changes electricity
to light! Long leg = (+),
Short leg = (-)



Buzzer — The Calling Bell!

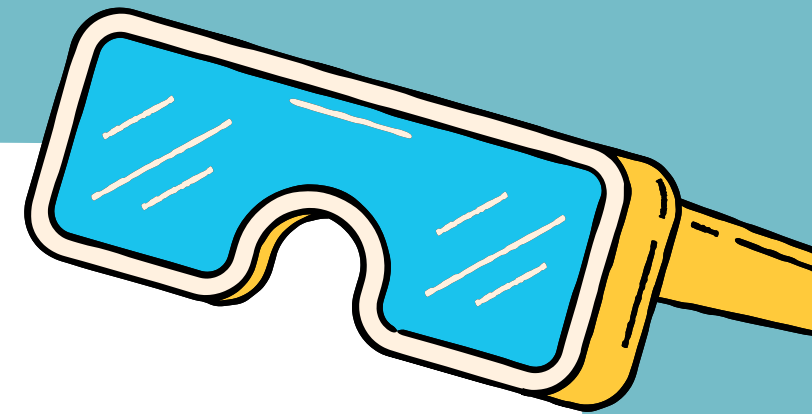

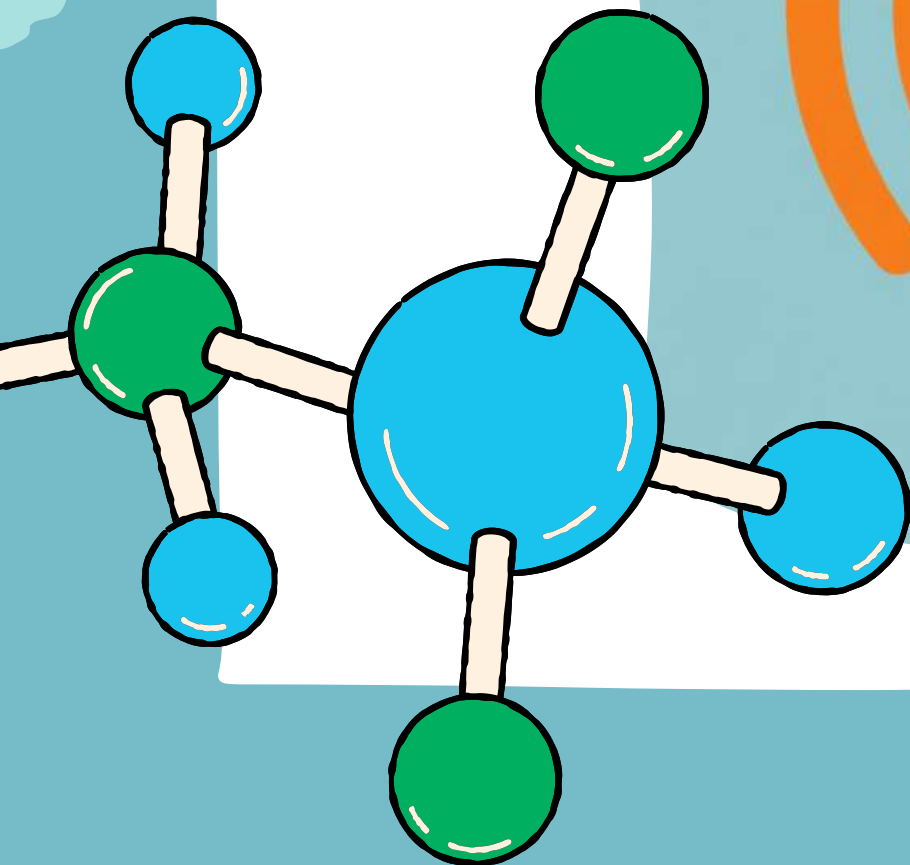Buzzer is like a
calling bell or
scooter horn.
Electricity makes
the buzzer BEEP!




Closed vs Open Circuit!



Closed Circuit ✓

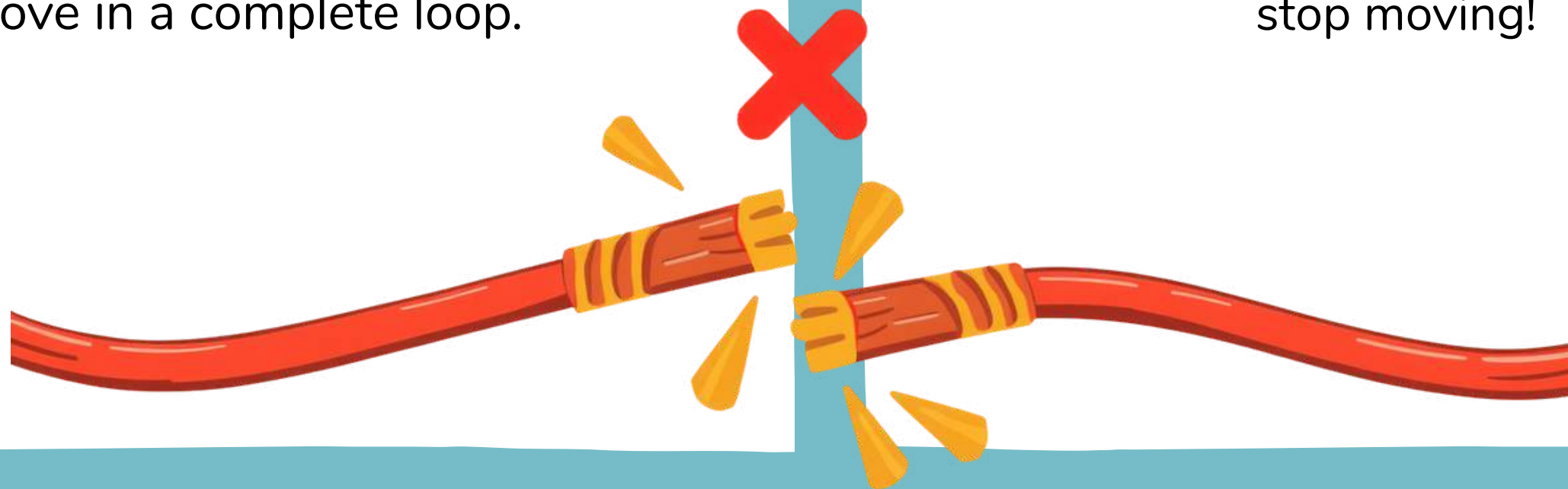Electricity flows! 💡 LED glows green and buzzer goes BEEP! Golden dots move in a complete loop.




Open Circuit ✗

Electricity stops! 🔌 Wire is broken — LED is off, buzzer is silent. Dots stop moving!




Polarity — Train Tracks!

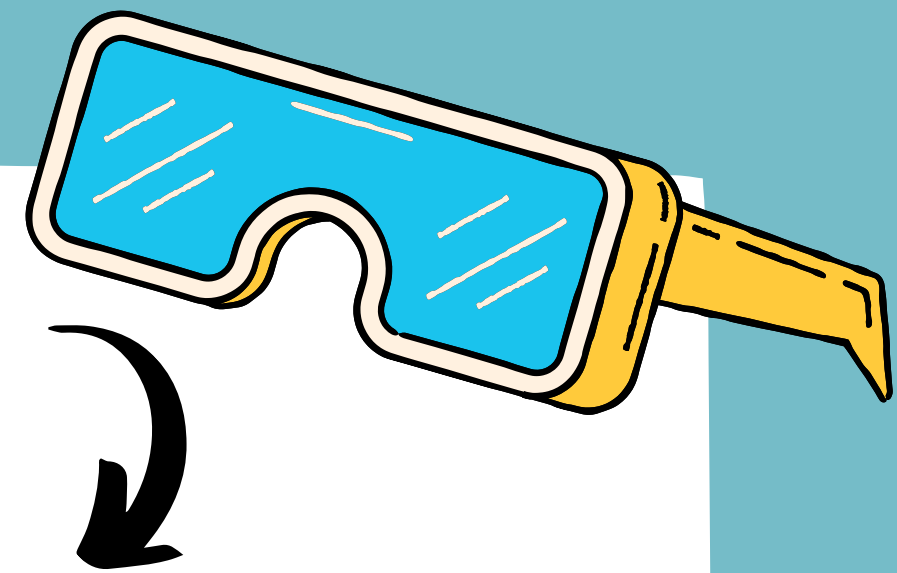


Correct!

Wrong!

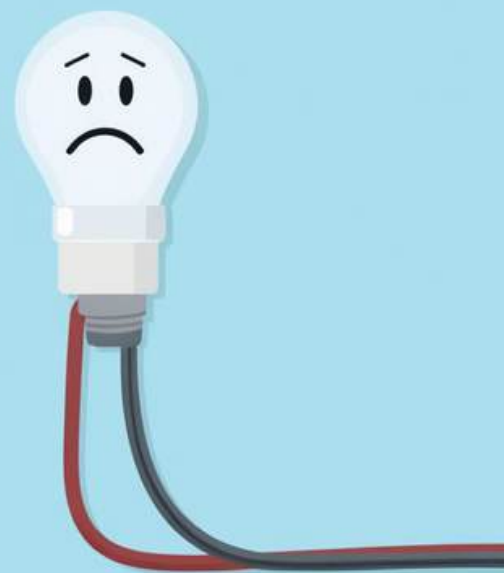

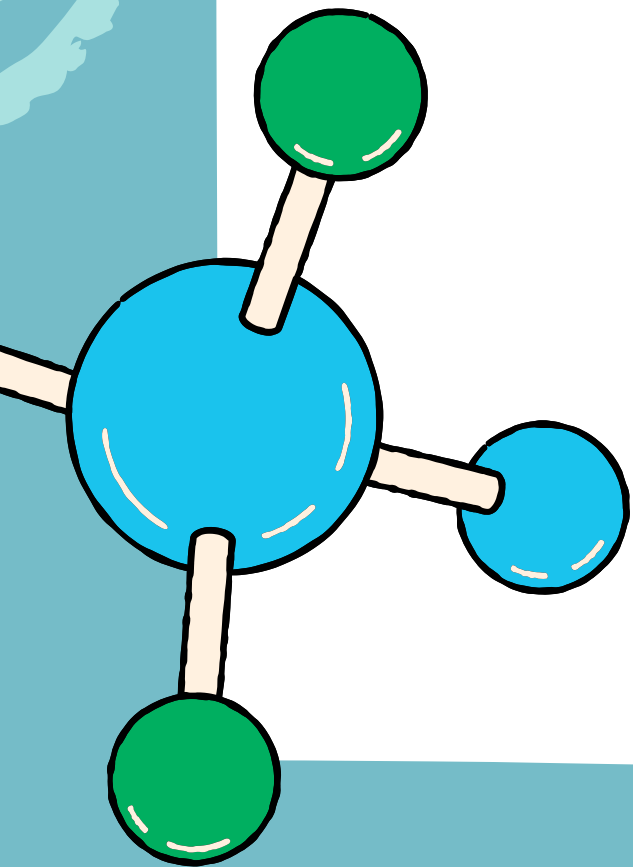Can you spot
the right way?
Long leg (+) in,
short leg (-)
out!






Step 1 — Place the Battery

Put the battery on your workspace.
Wow, you just started your circuit!




Step 2 — Connect LED to Battery (+)

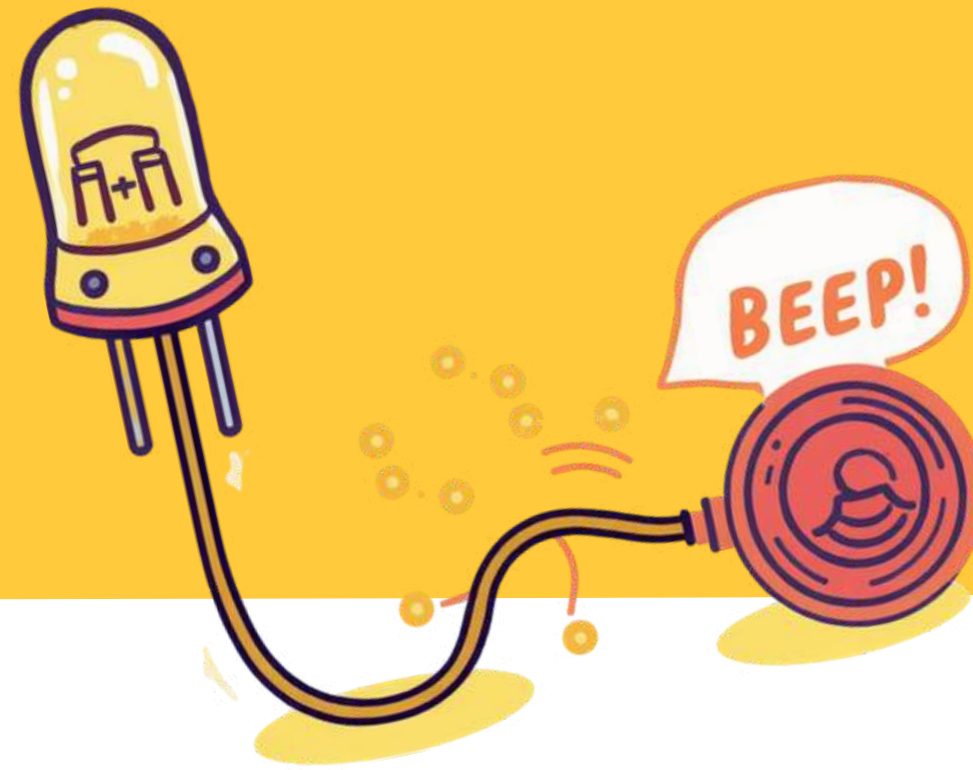Connect the red wire from battery (+)
to the LED long leg (+). Great job!
Electricity can flow now! ⚡



Step 3 — Connect LED to Buzzer (+)

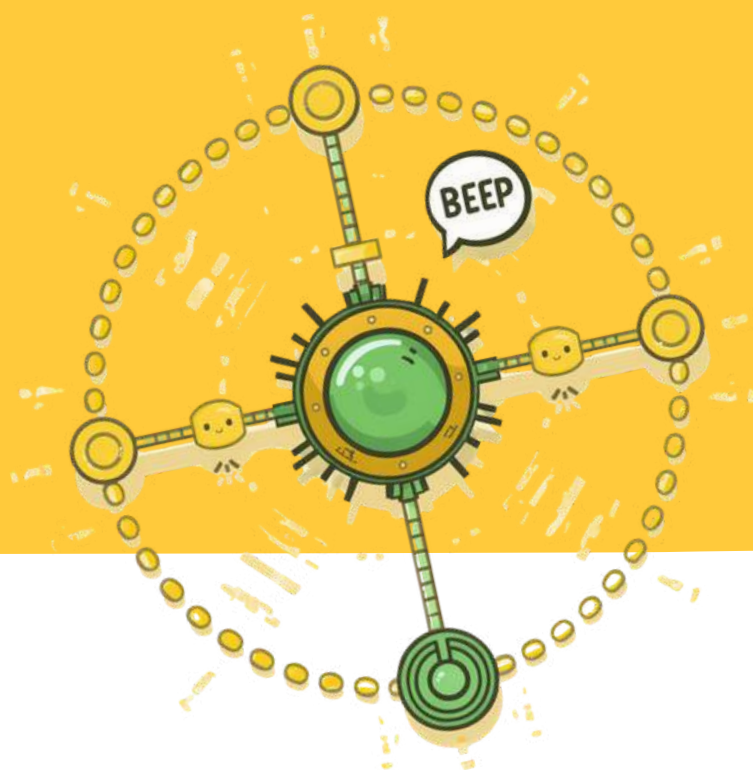Connect LED short leg (–) to buzzer red wire (+).
Glowing dots keep flowing... "BEEP!" Almost there!



Step 4 — Complete the Loop!


Connect buzzer black wire (–) to battery (–).

Wow, you just made electricity move! 🎉


LED glows green & buzzer beeps — circuit complete!

SAFETY FIRST!

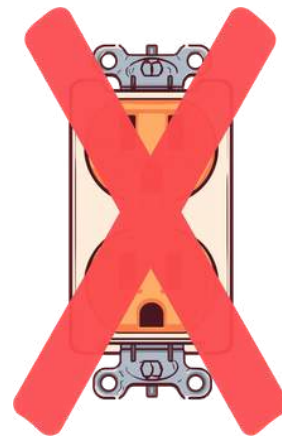
Always use toy batteries (3V or 9V) — never bigger ones!
Never touch wall sockets or main power points. Ask a grown-up for help!



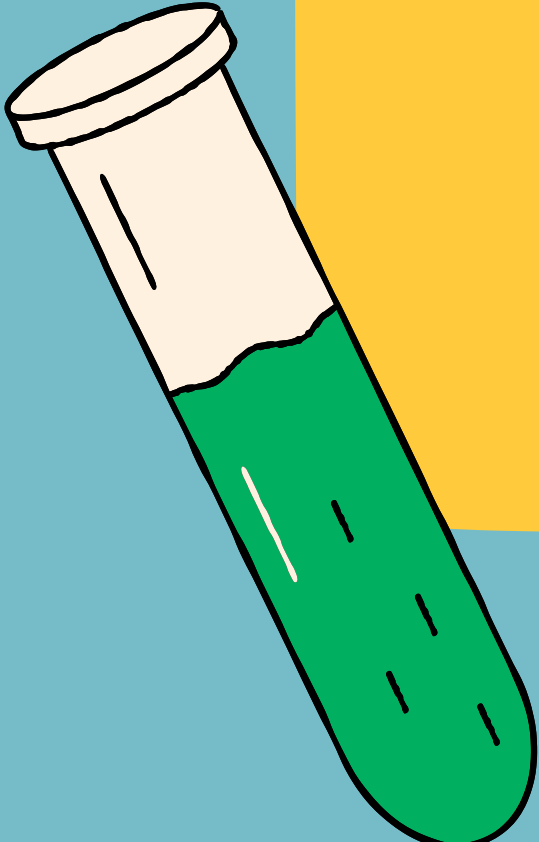Stay safe, stay curious, and keep inventing! ⚡



What We Learned Today!

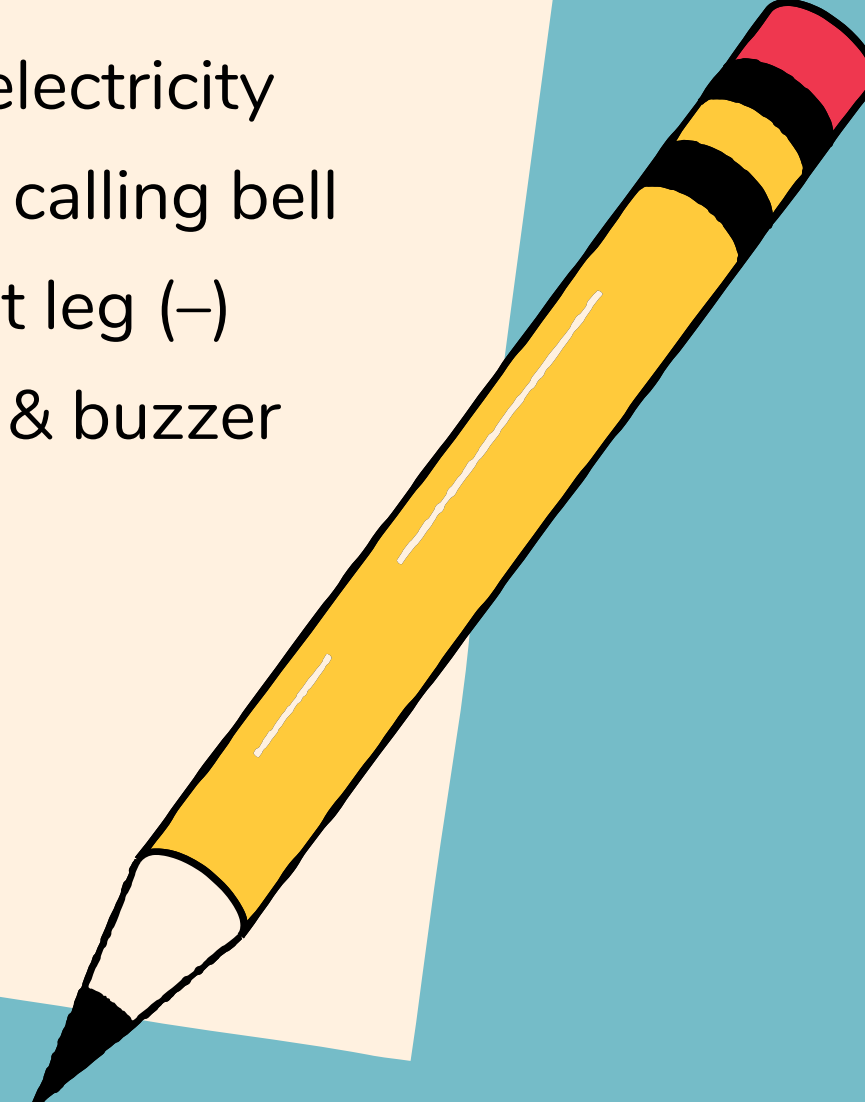-  Battery pushes electricity like a water tank
 -  Circuit is a closed loop for electricity
 -  LED = festival light; Buzzer = calling bell
 -  Polarity: long leg (+), short leg (-)
 -  Closed circuit = LED glows & buzzer beeps!
- 

You Are a Circuit Champion!

KEEP EXPLORING AND INVENTING!

