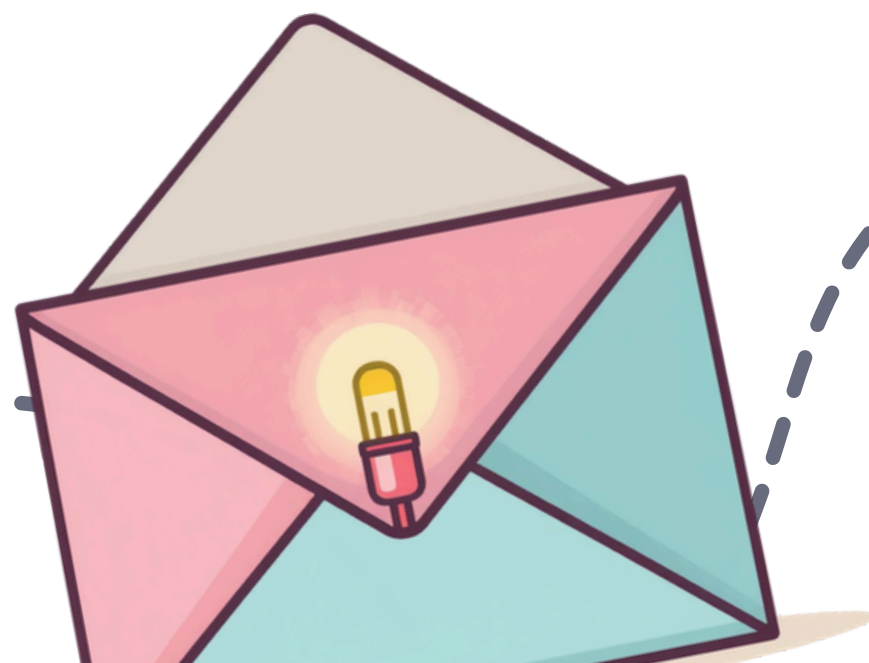




**Paper Circuit —
LED Greeting Card
Learn How to Light Up
Your Creativity!**





What is Electricity?



- Electricity is a kind of energy that makes lights turn on!
- ⚡ Powers lights and lamps
- 🔋 Makes toys work
- 📱 Runs gadgets and devices



What is a Circuit?

A circuit is a path that electricity follows.

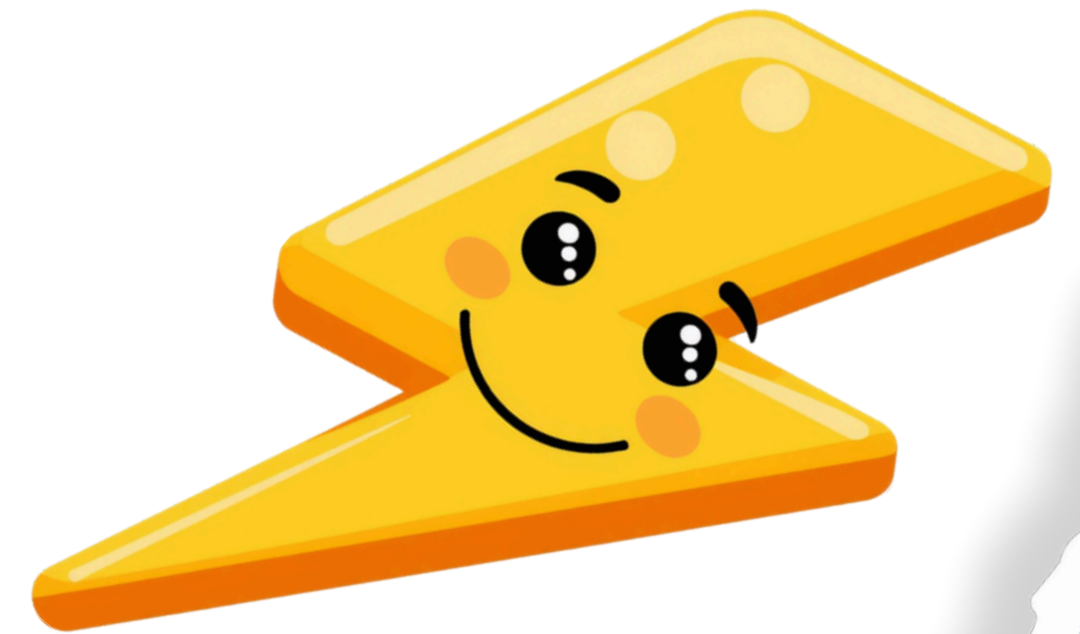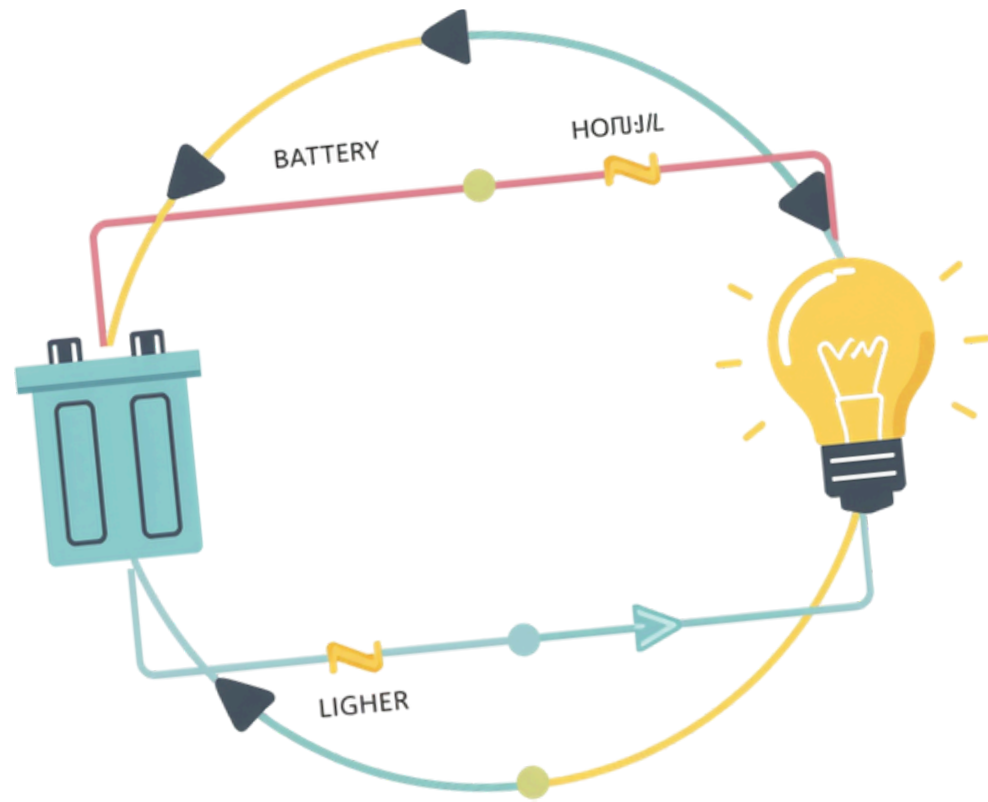
- Battery → gives the power
- Wire (or copper tape) → carries the electricity
- Light (LED) → lights up when electricity flows through!






Meet the Paper Circuit

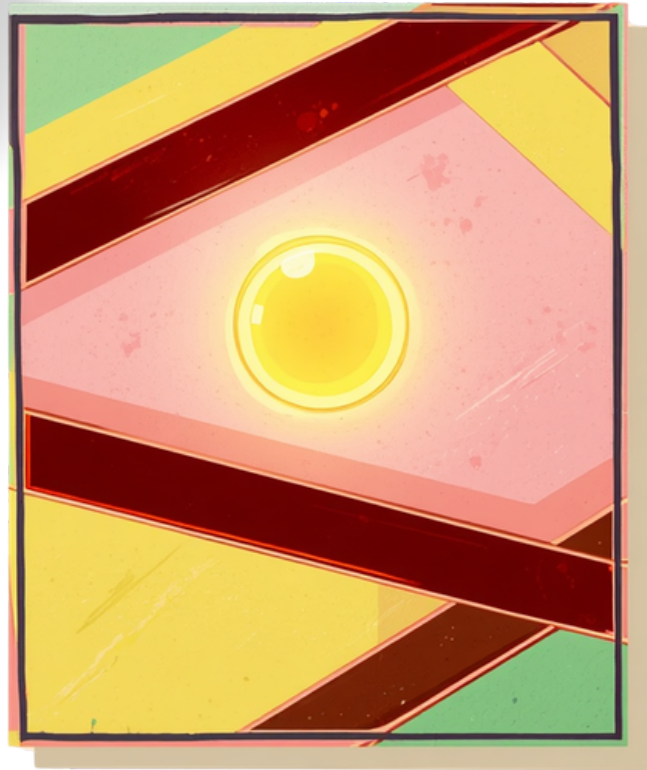A paper circuit is a fun way to make lights using paper! It uses simple materials and is very easy to make.
Anyone can do it!



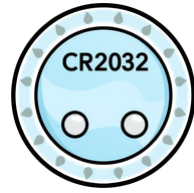


Components You Need

-  LED Light
-  Copper Tape
-  Coin Cell Battery
-  Paper or Cardstock



How Electricity Flows

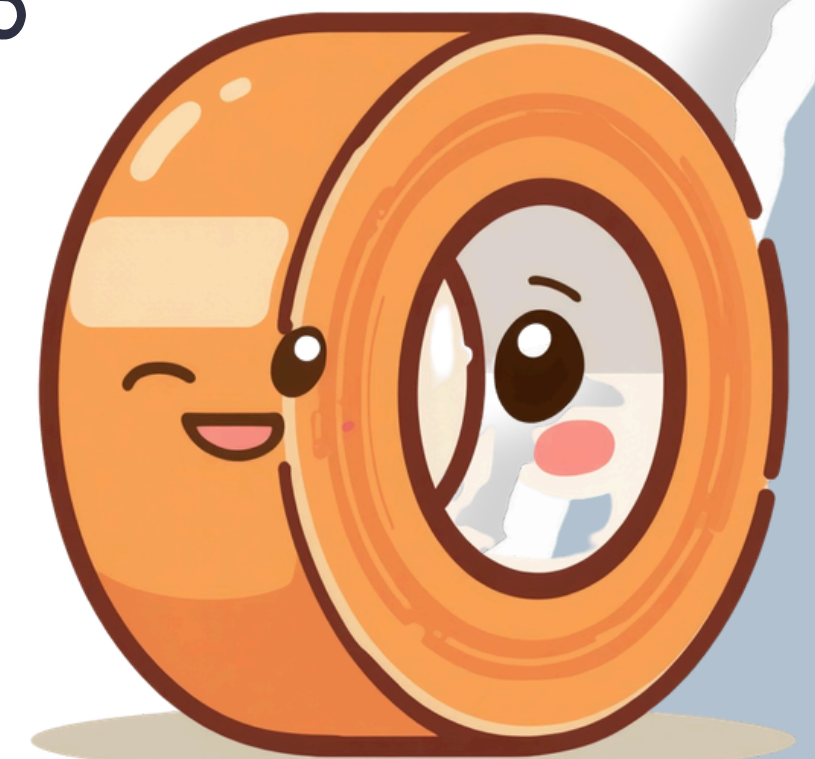Electricity moves from the battery, through the copper tape, to the LED light, and back to the battery — completing the circuit!






Safety First!



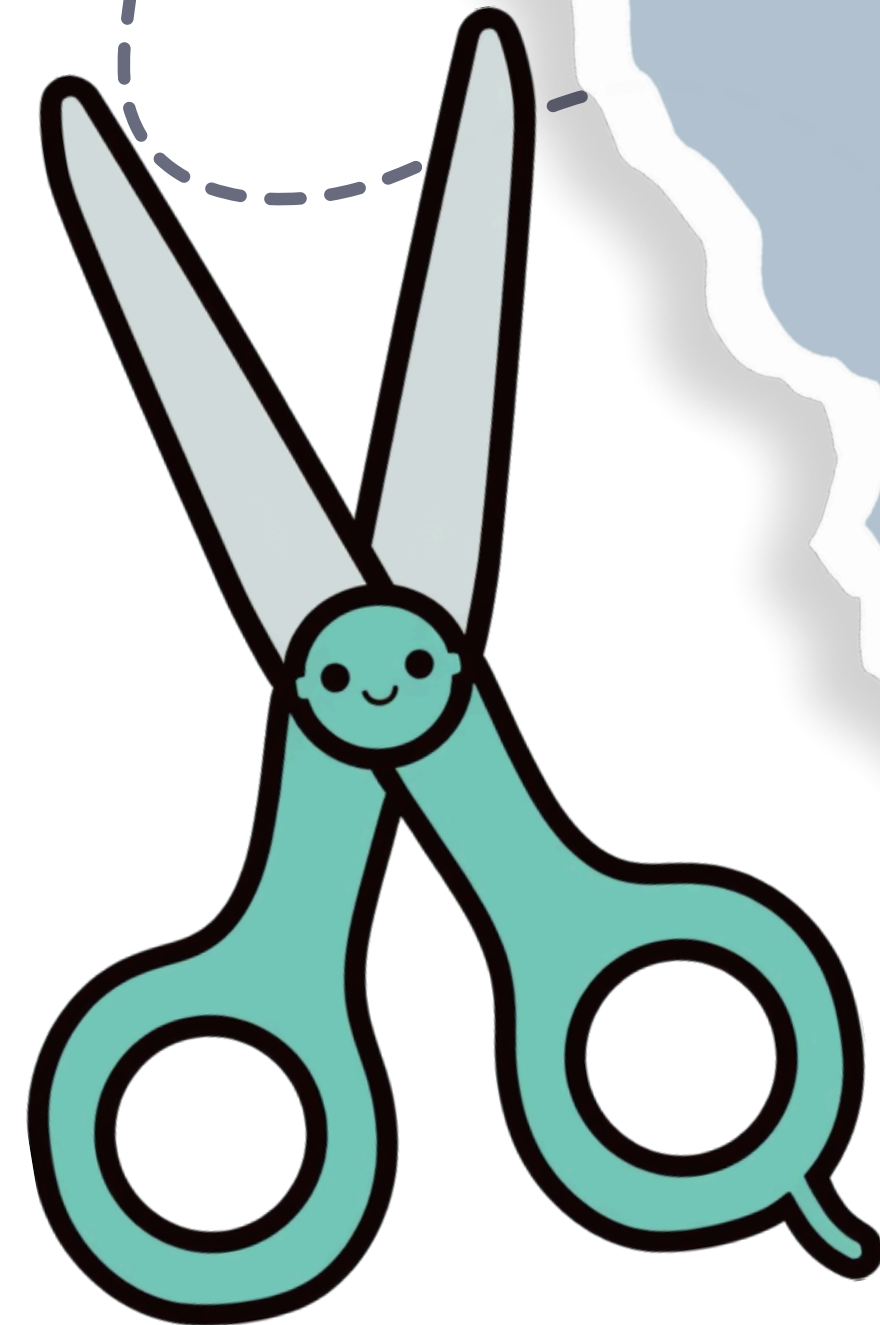- 🛡️ Always ask an adult for help
- 🔋 Don't touch batteries for too long
- ✂️ Use scissors carefully with adult supervision
- 💧 Keep circuits dry and clean






Step 1: Prepare Your Paper


Choose your paper or cardstock and fold it like a greeting card.

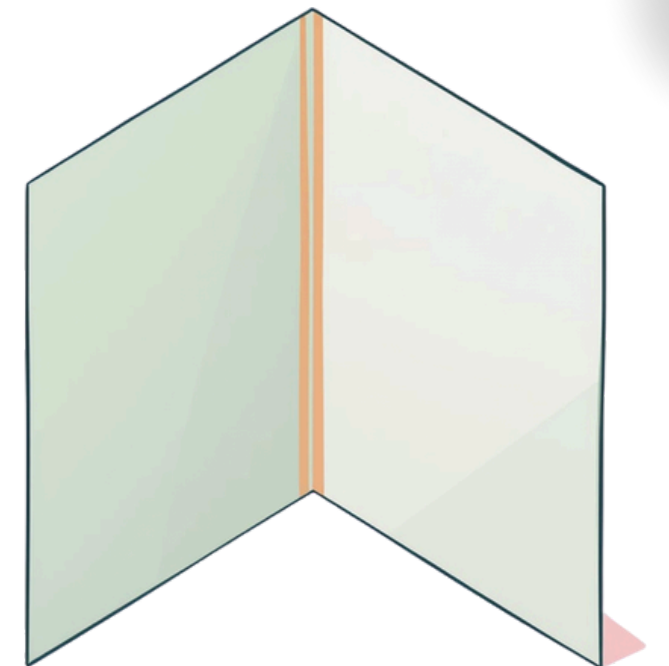- Pick a thick paper or cardstock
- Fold it in half neatly
- Make sure the fold is crisp and clean




Step 2: Add Copper Tape

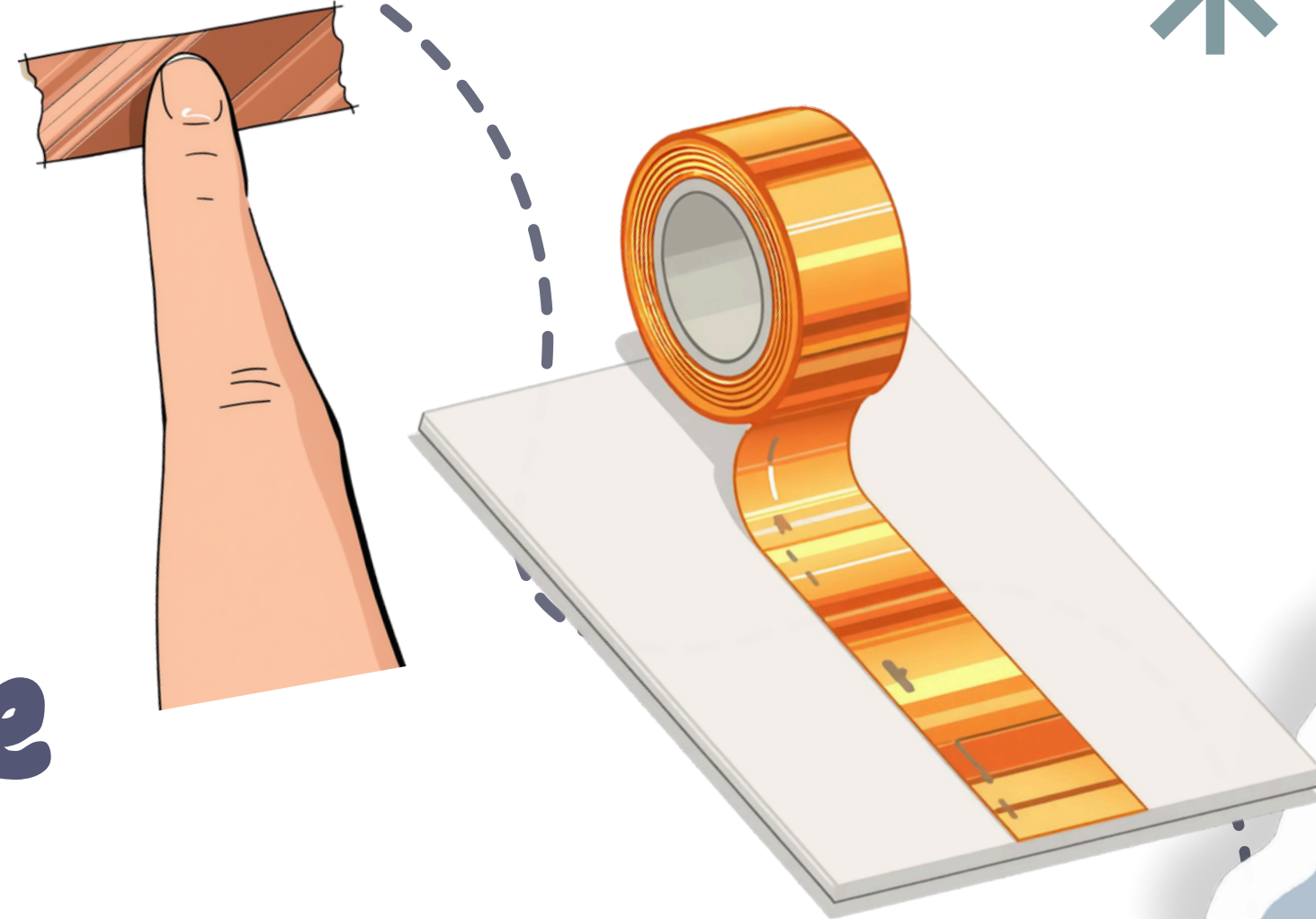- Stick copper tape on the paper to create the path for electricity.
- Press the tape down firmly as you go
- Keep the tape in a straight, connected line
- Don't let the tape overlap or cross!



Step 3: Place the LED Light

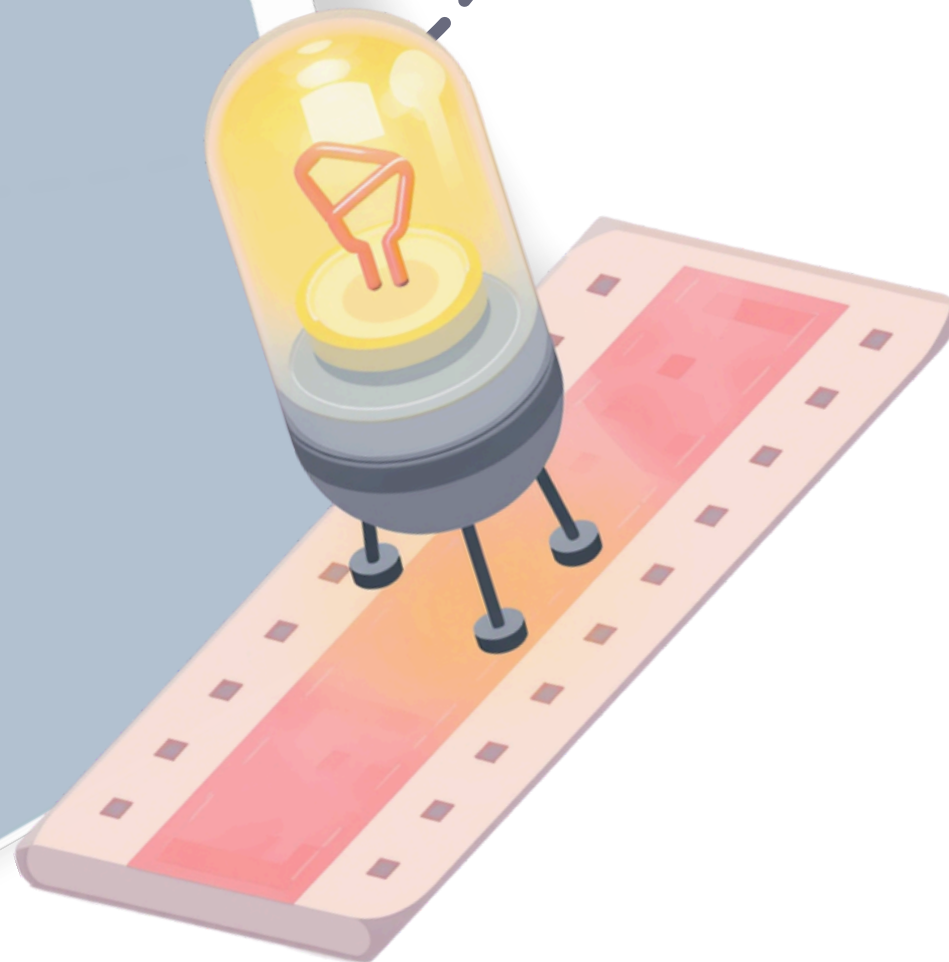
- Put the LED on the copper tape. Make sure the legs are placed correctly!
-  Do: Long leg on + side  Do: Short leg on – side
-  Don't: Mix up the legs!




Step 4: Add the Battery

Put the coin cell battery under the copper tape to complete the circuit.


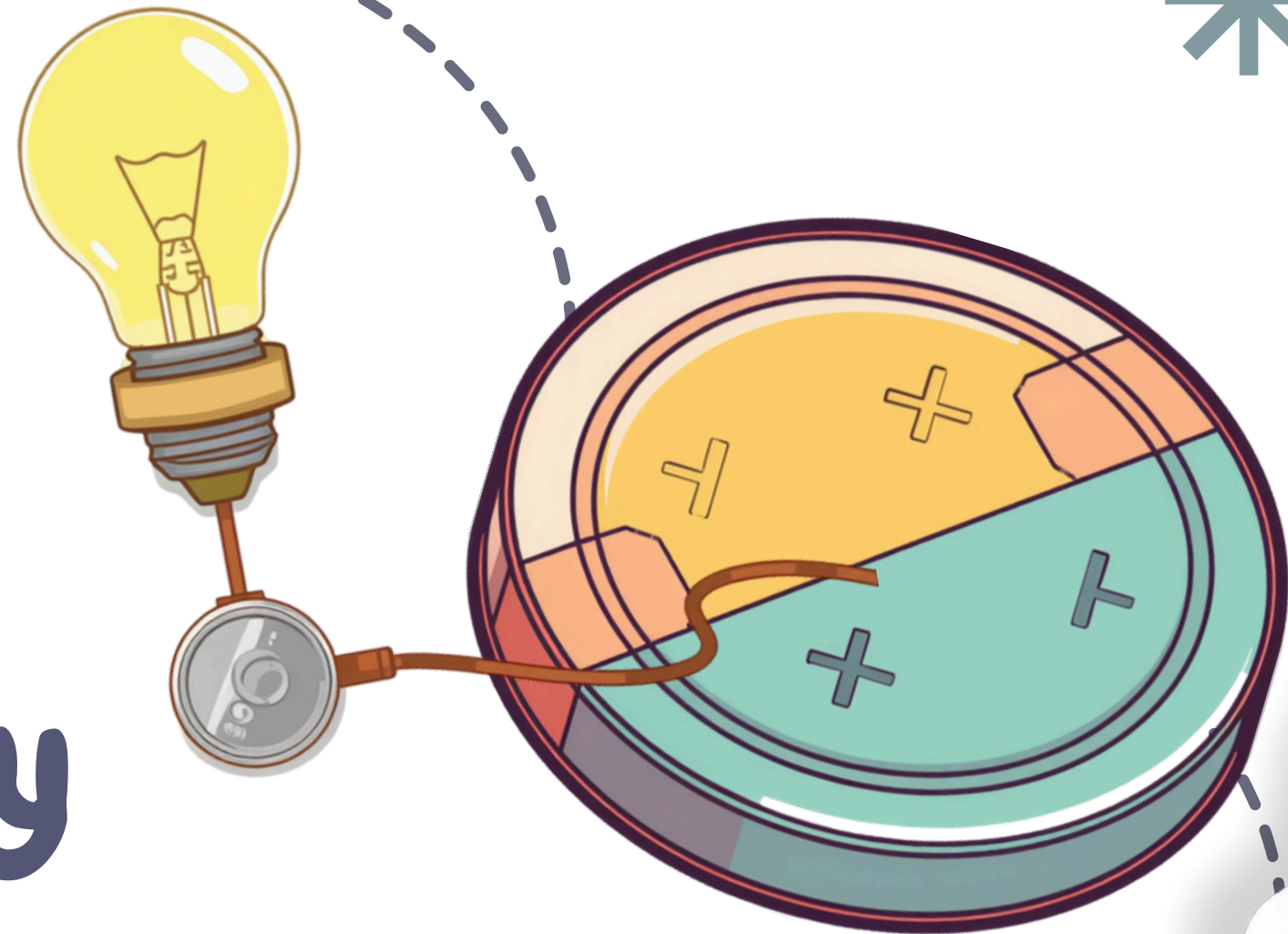
- Place battery with + side facing up
 - Press tape firmly over battery
 - Test if your LED light turns on!




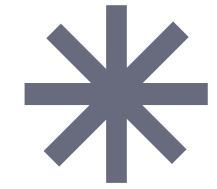

Step 5: Decorate Your Card!

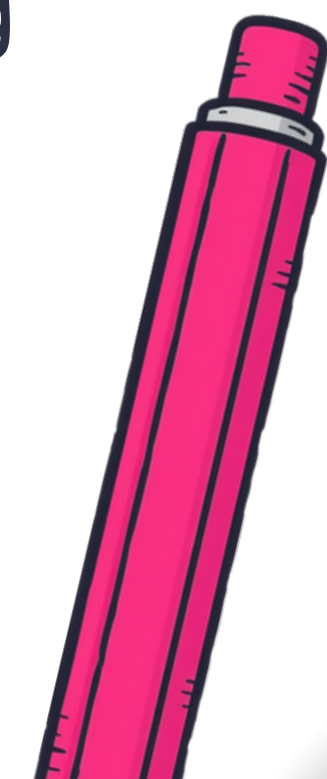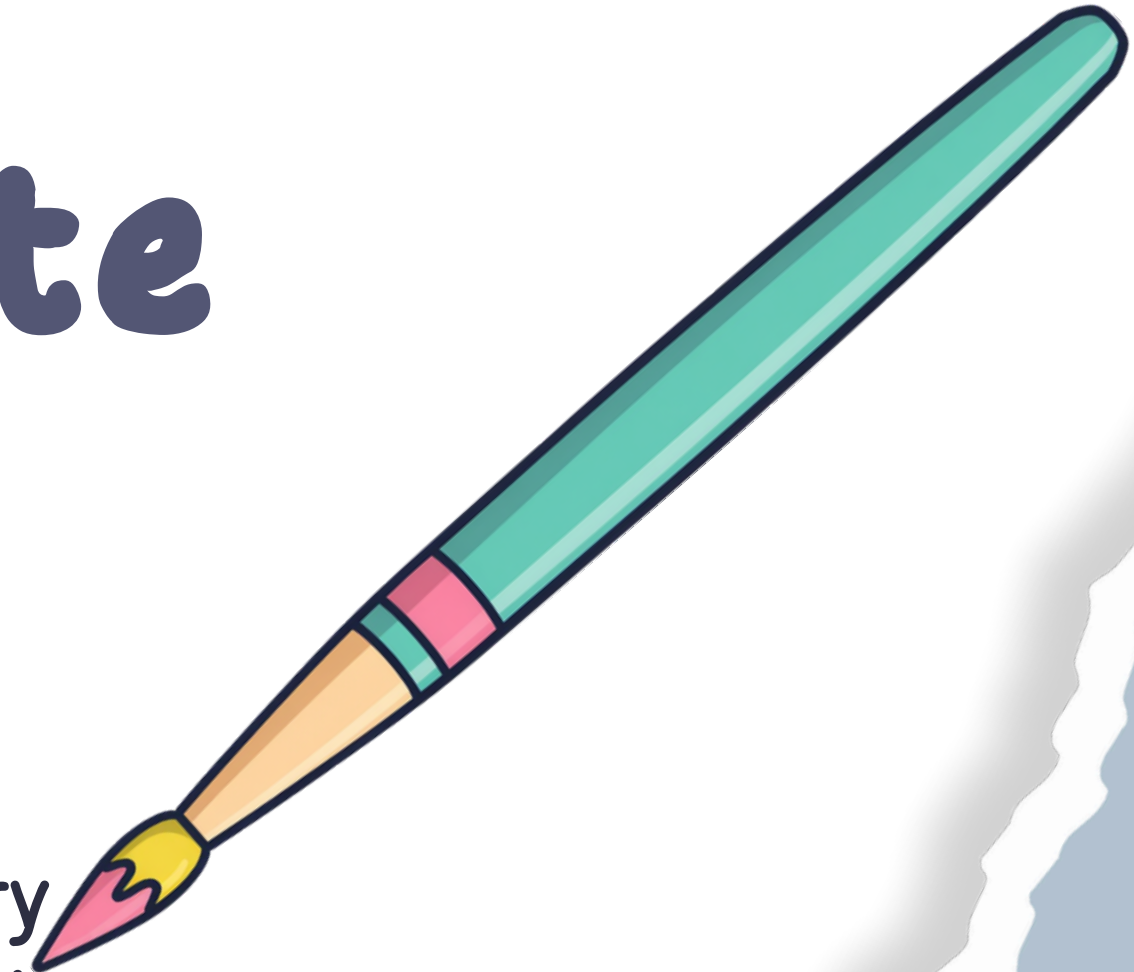Make your card beautiful and unique! Try drawing, adding stickers, colouring, or writing a special message. Let your creativity shine!



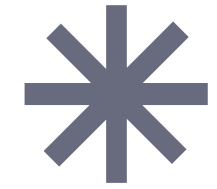

Troubleshooting Tips




- 💡 Light not turning on? Check your tape connections!
- 🔋 Make sure the battery is fresh and placed the right way.
- ✅ Ensure both LED legs are touching the copper tape well.
- 😊 Don't give up — try again, you've got this!






Fun Facts About LEDs and Circuits!

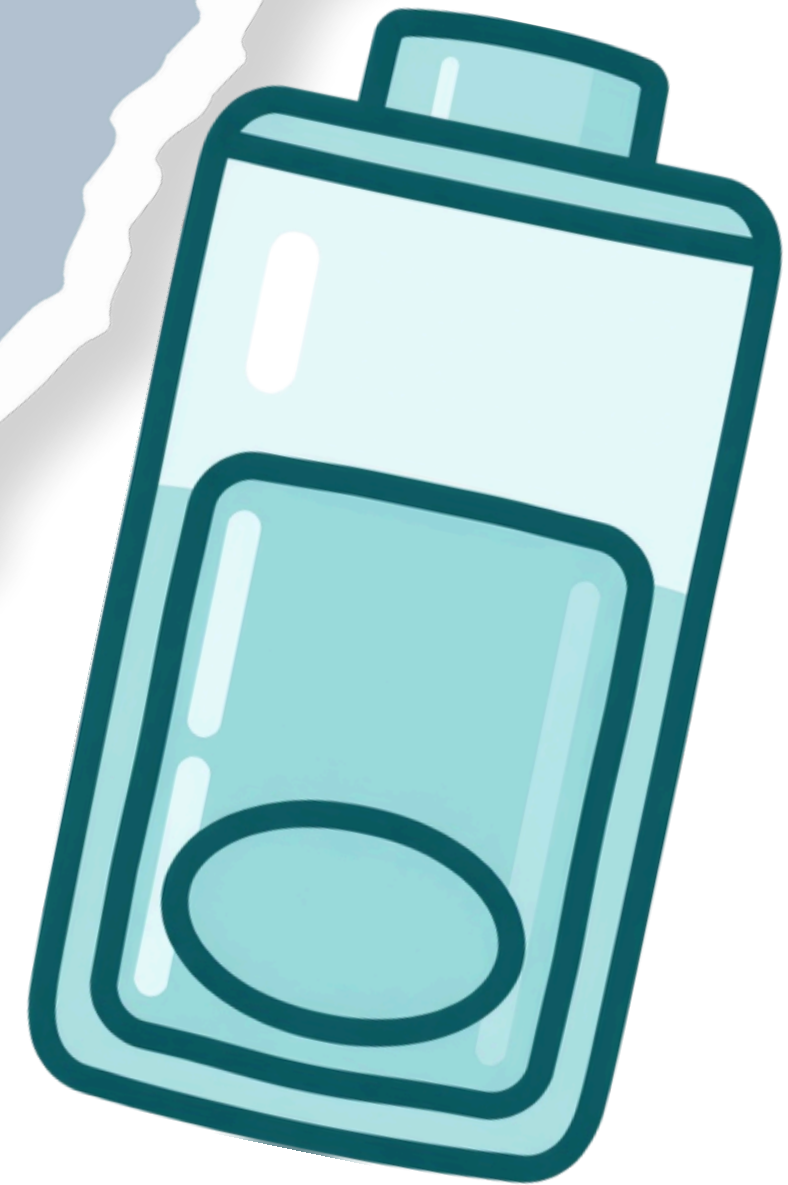

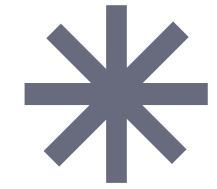- 💡 LEDs use less energy than regular bulbs!
- 🔌 Circuits are found in toys, phones, and cars!
- abc "LED" means Light Emitting Diode!





Creative Project Ideas




Make birthday cards with blinking lights



Create holiday decorations with paper circuits



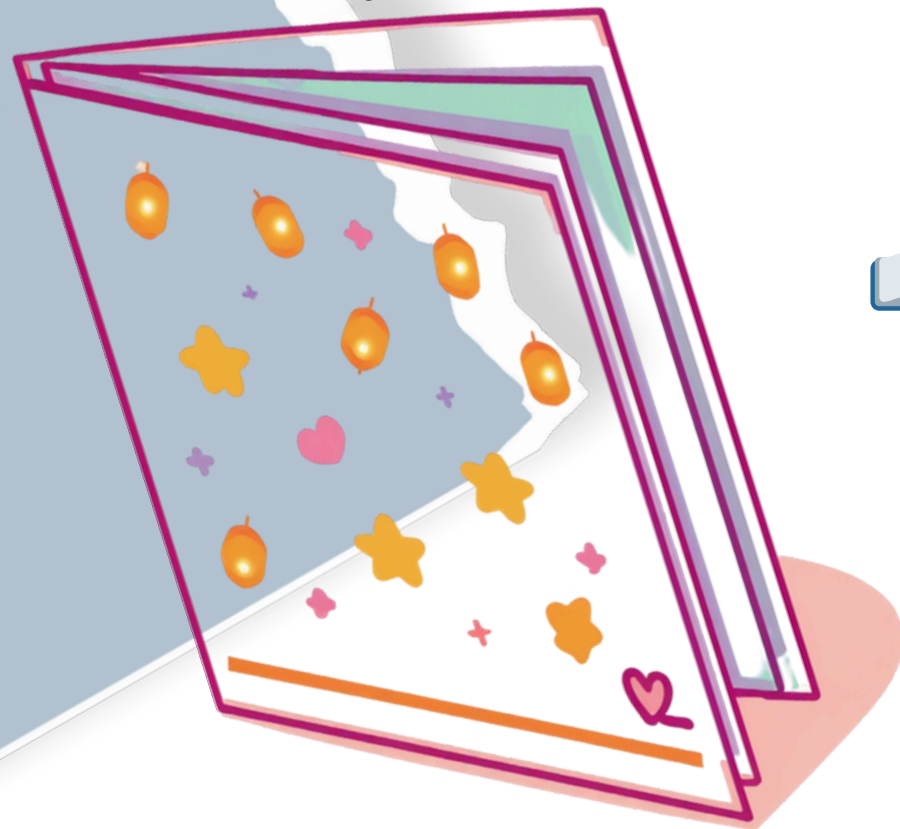Design your own storybook with light-up pictures



Thank You!

Thank you for joining us today! Any questions? Keep shining and keep learning!

