

Circuit Basics — What is a Circuit?

Grade 2 | Hardware




What is Electricity?

Electricity is the power that makes lights, fans, and TVs work!



What is a Circuit?

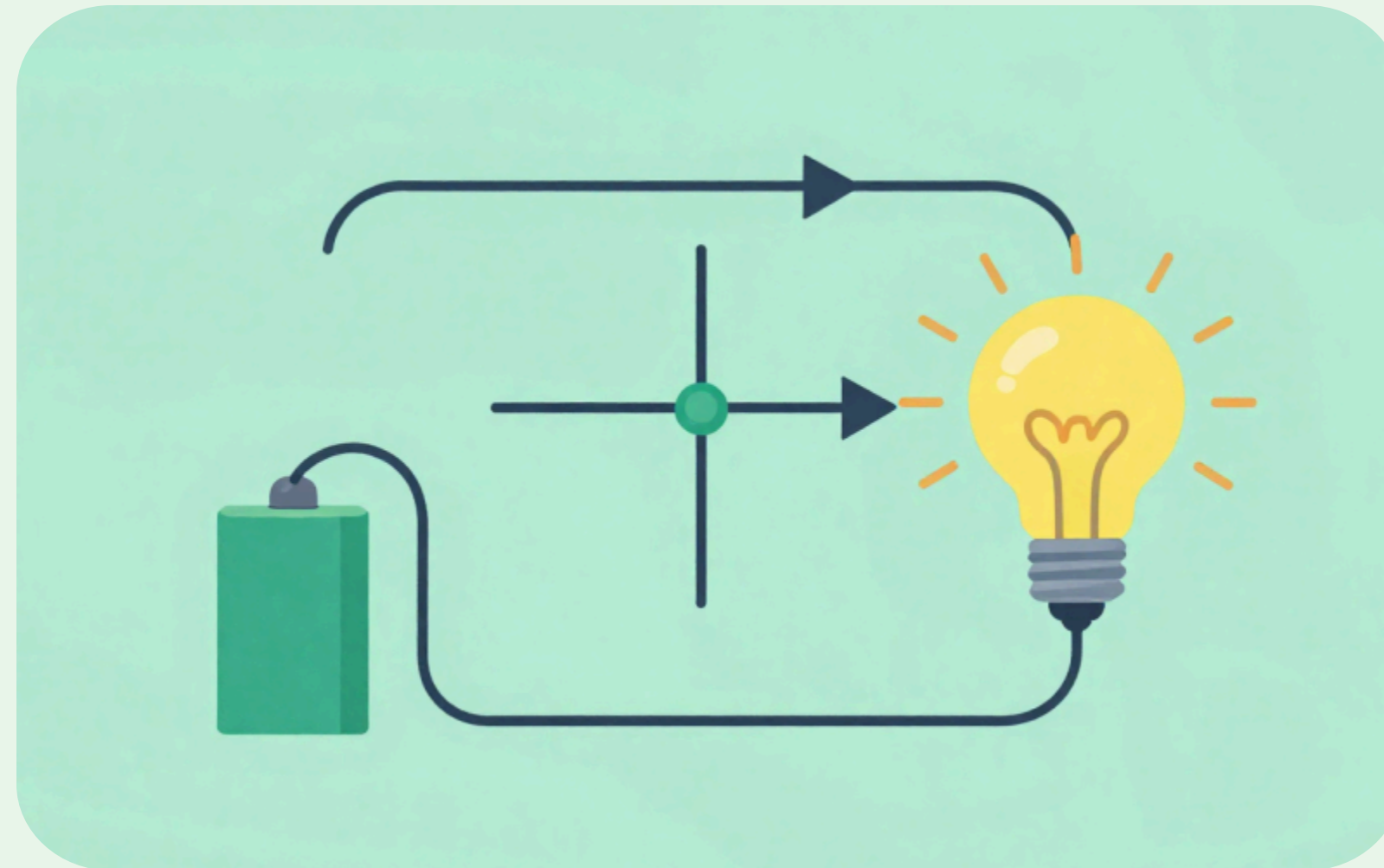A circuit is a path that lets electricity flow to make things work.




Parts of a Circuit

Battery — Gives electricity

Wires — Carry electricity


Bulb — Uses electricity to shine

Switch — Turns electricity on and off

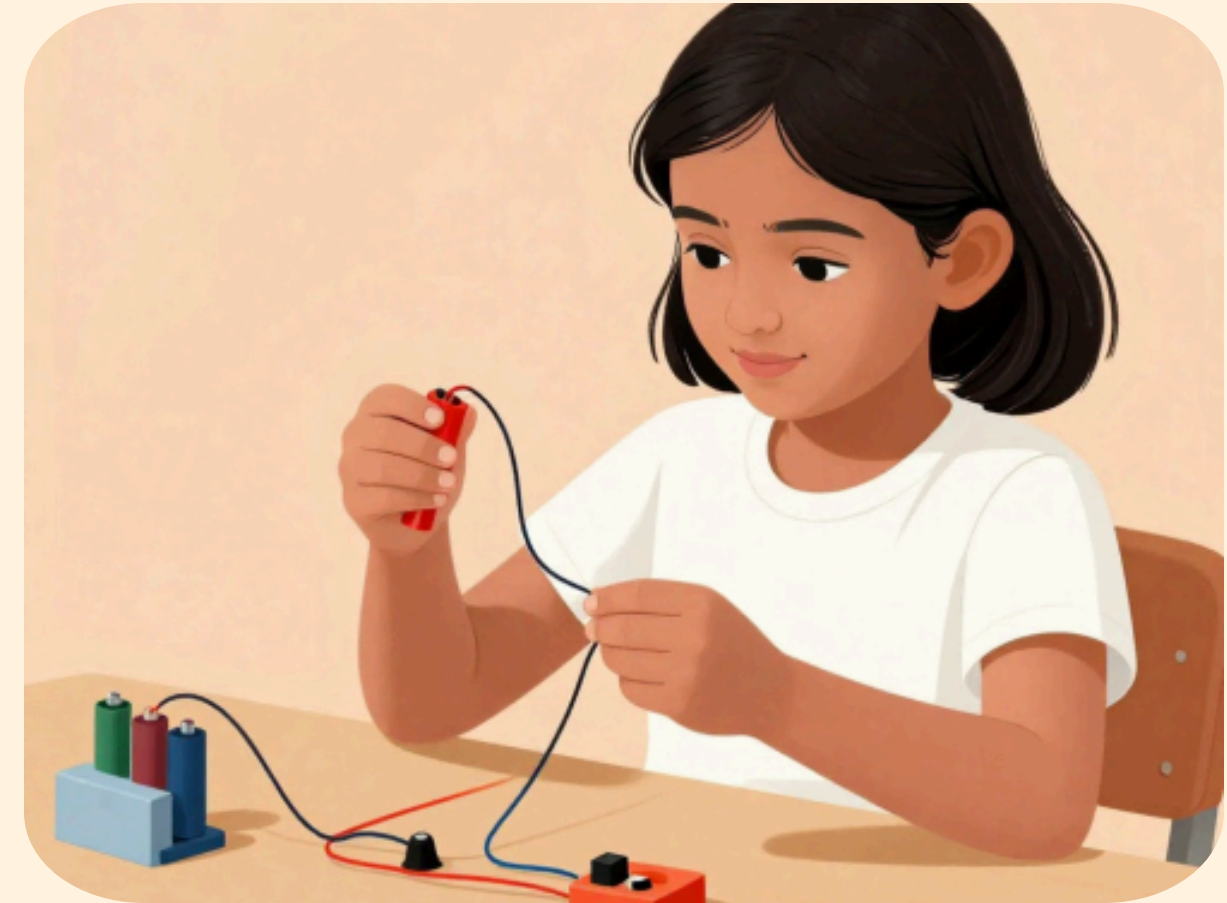



How Does a Circuit Work?

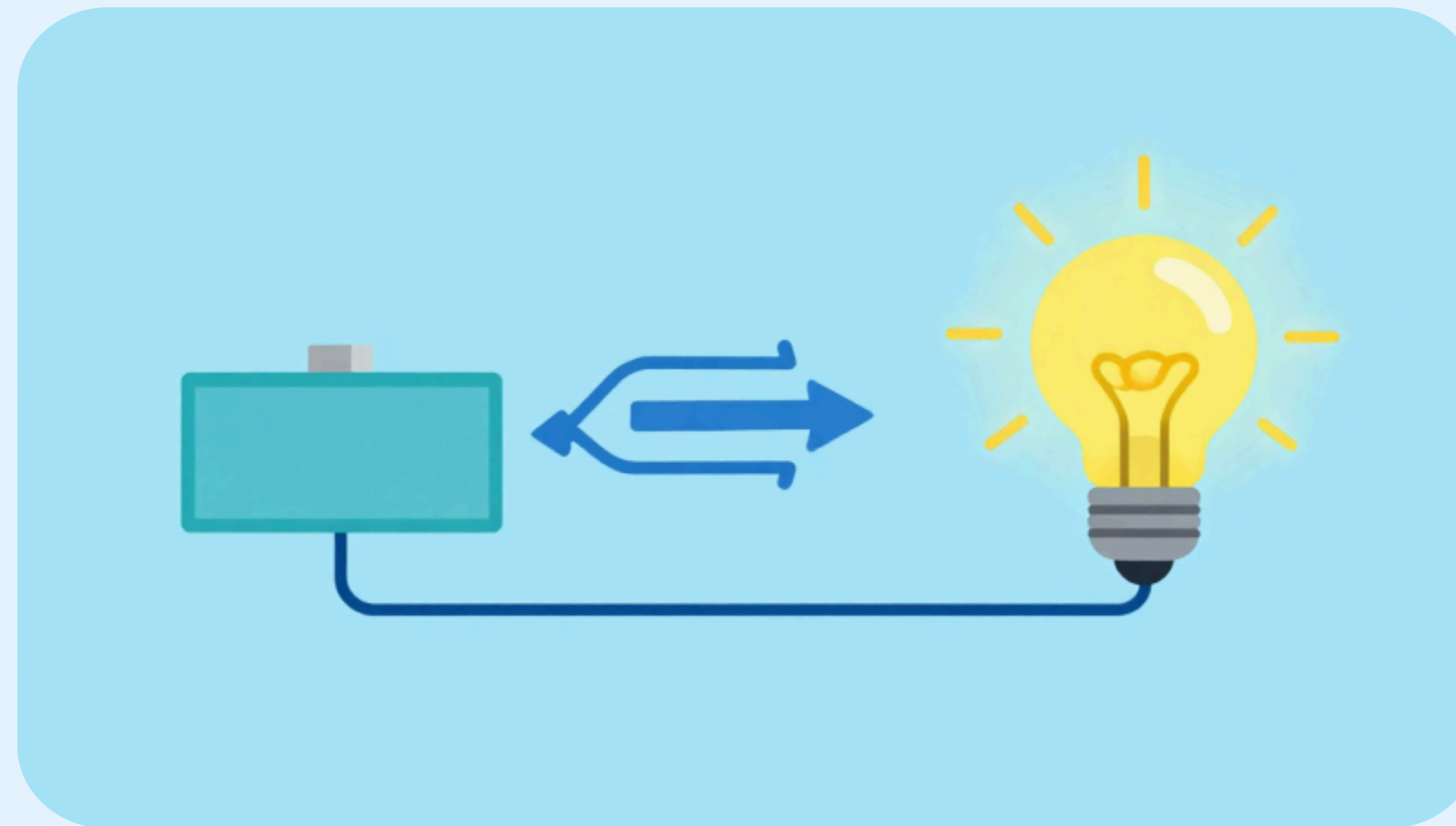Electricity travels from the battery, through the wires, to the bulb, and back to the battery.




Closed Circuit vs Open Circuit

Closed = electricity flows, bulb lights up | Open = electricity stops, bulb is off

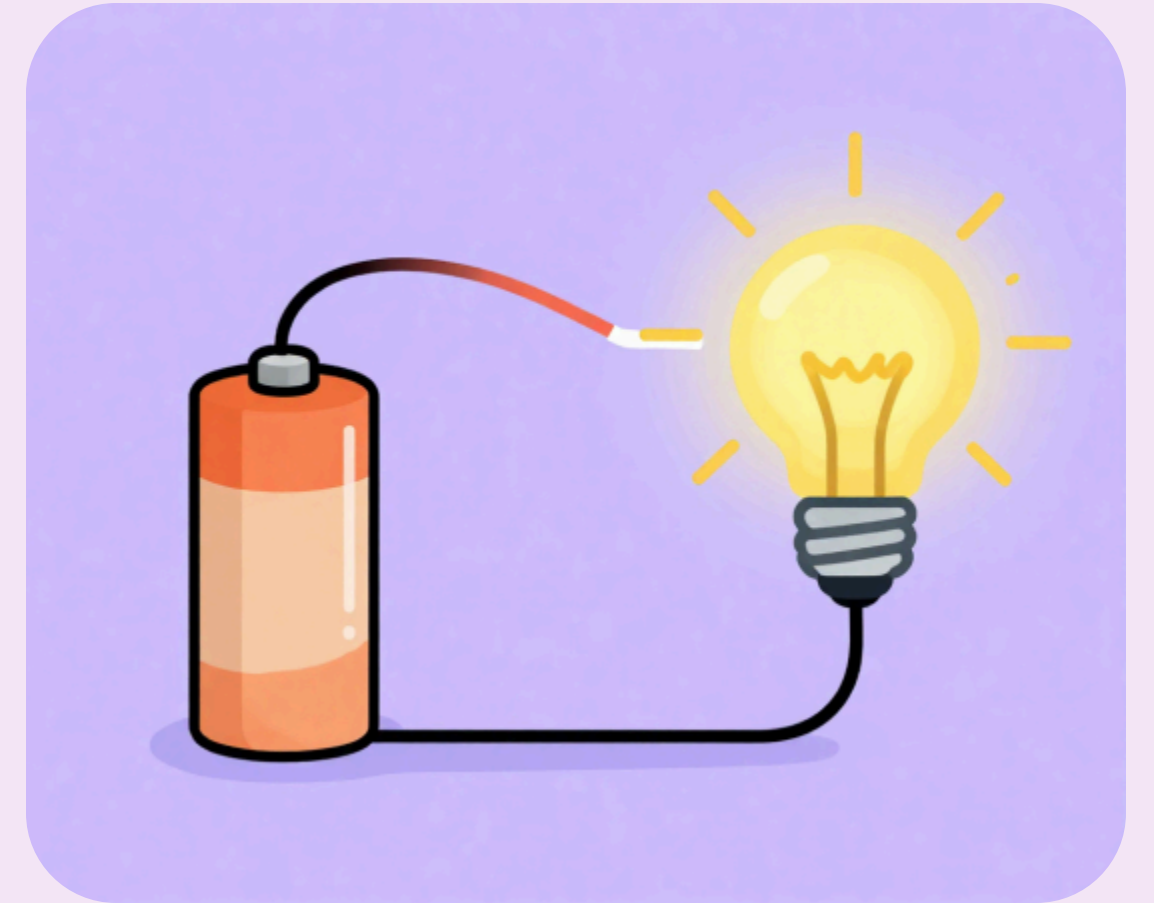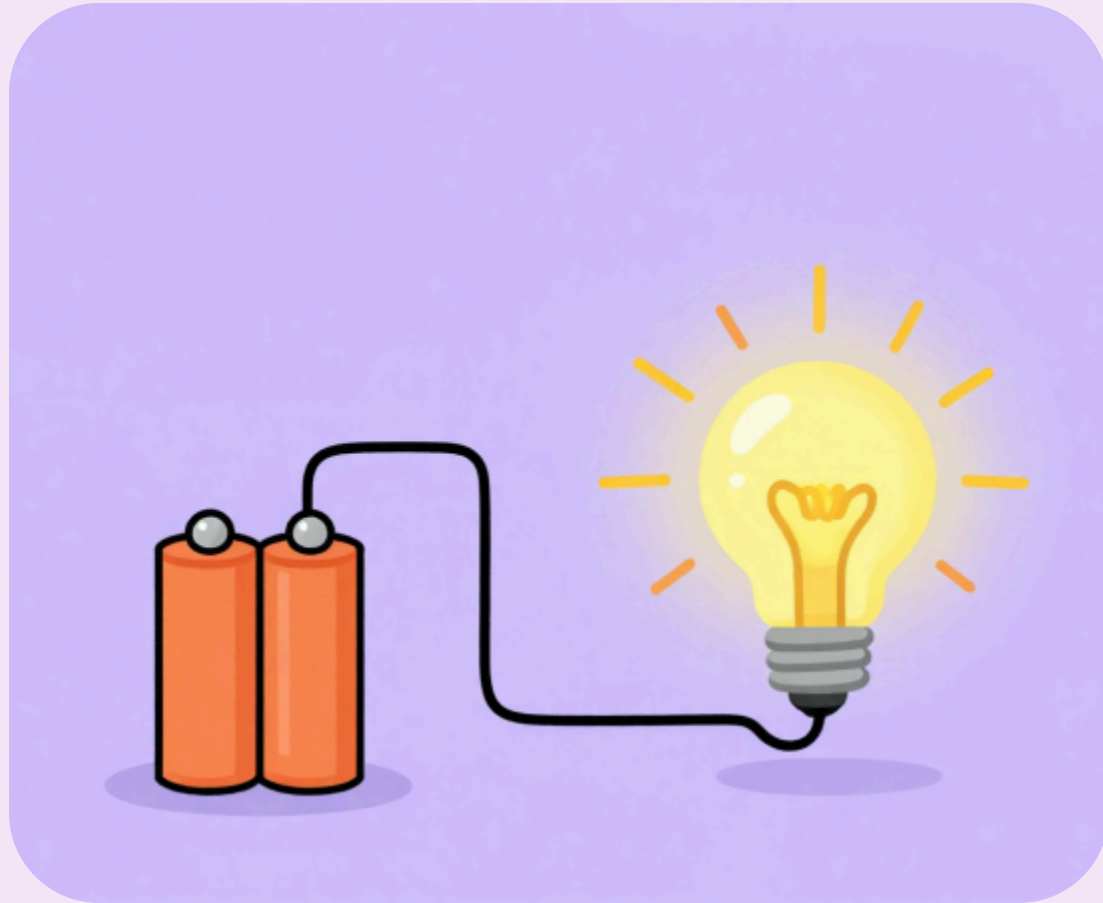

Everyday Circuits Around Us

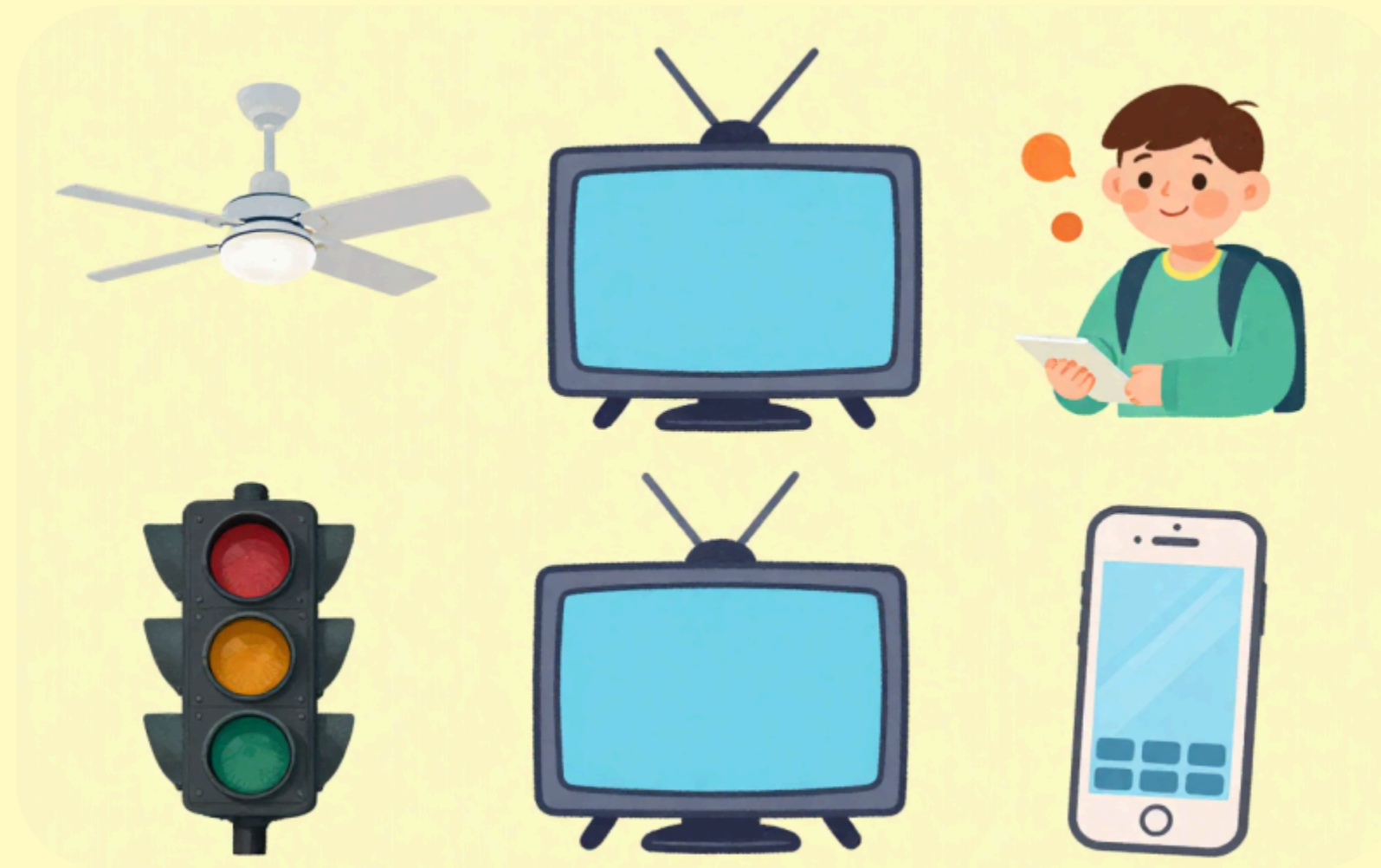Circuits help many things work every day!



Why Circuits Are Important

They help us see light
They make machines work
They power our homes
They keep us connected



Let's Make a Simple Circuit!

Step 1: Take a battery

Step 2: Connect wires

Step 3: Add a bulb

Step 4: Watch the bulb light up!



Circuit Safety Tips

Don't touch wires when plugged in

Always ask an adult for help

Keep circuits dry

Turn off the switch when not using




Fun Facts About Circuits!

The first electric circuit was built over 200 years ago!

Circuits are in almost all electronic devices.

Some circuits are tiny and fit inside phones!

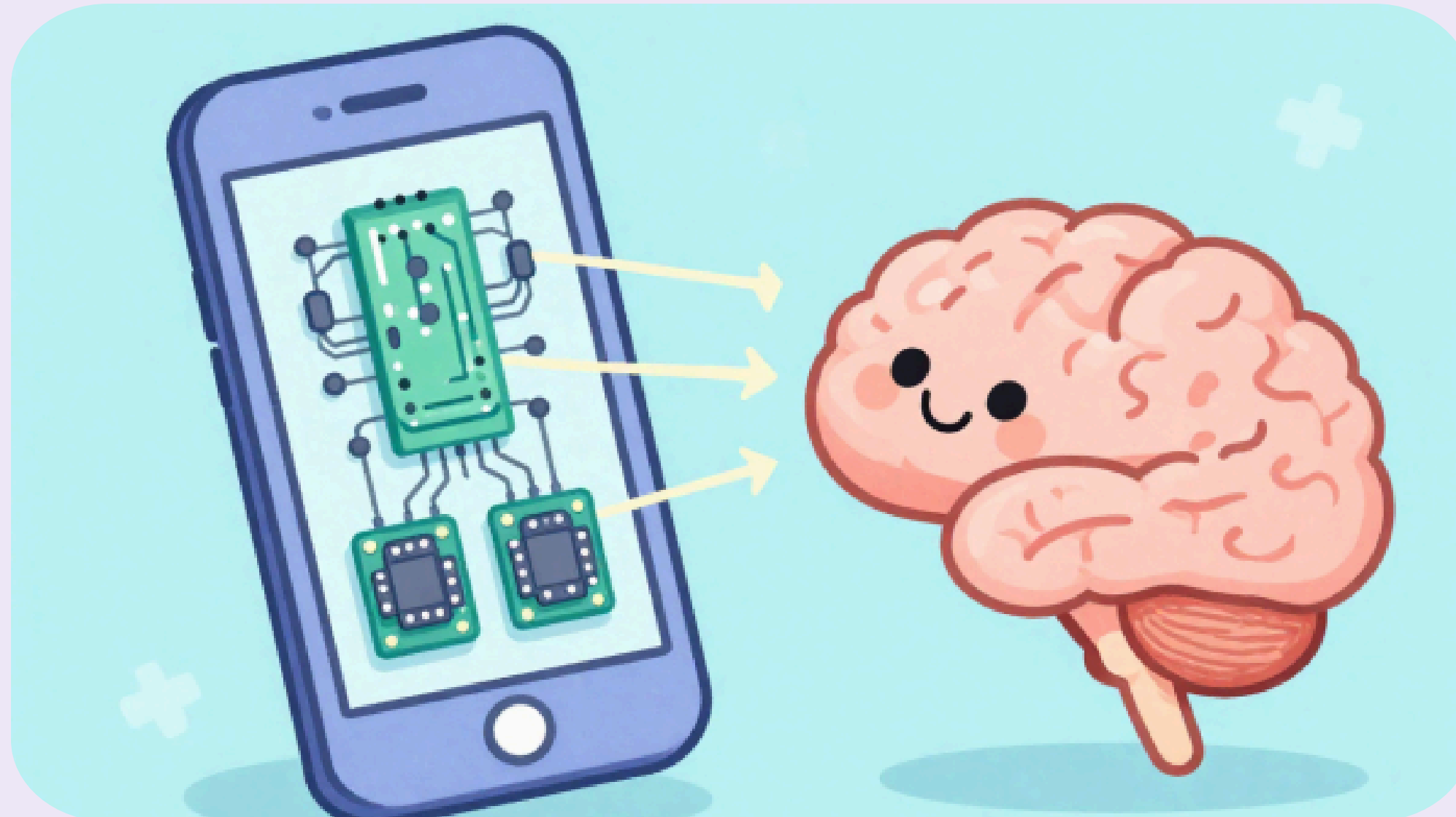Your brain uses tiny electric signals too!



Summary & Thank You!

A circuit is a path for electricity.

Circuits need batteries, wires, bulbs, and switches.

Circuits make many things work around us.

Always be safe with electricity!

