

Arduino & External LEDs

Learn & Light Up!

A Fun Electronics Lesson for Grade 5

- Discover how Arduino, LEDs, and resistors work together
 - Learn to build your very first light-up circuit
- Test your knowledge with a 20-question quiz at the end!

Name: _____

Class: _____

■ Lesson: Getting to Know Arduino & LEDs

■ What is Arduino?

Arduino is a tiny computer that helps us control lights, motors, and more! It lets us make cool projects with electronics and coding.

■ What is an LED?

LED stands for **Light Emitting Diode**. It is a special light that glows when electricity passes through it.

■ Why Use External LEDs?

- Brighter light
- Different colors available
- Can be placed anywhere in a project
- More fun to build circuits!

■ What is a Resistor?

A resistor controls the amount of electricity flowing in a circuit. It keeps our LED safe!

■ Why Do We Need Resistors?

Without Resistor	With Resistor
LED might burn out! Too much electricity can damage it.	LED stays safe and glows just right! Perfect brightness.

■ How to Calculate Resistor Value

$$R = (V \text{ source} - V \text{ LED}) / I \text{ LED}$$

V source = 5V (Arduino voltage)

V LED = 2V (LED voltage)

I LED = 20 mA (current we want)

■ Example Calculation

$$R = (5V - 2V) / 0.02A$$

$$R = 3 / 0.02$$

$$R = 150 \text{ Ohms}$$

■ We need a 150 Ohm resistor!

■ How to Connect LED & Resistor to Arduino

- Connect the Arduino pin to the resistor
- Connect the resistor to the LED long leg (+)
- Connect the LED short leg (–) to GND
- Double-check before powering on!

■ Simple Circuit Diagram

Arduino Pin 13 → Resistor → LED → GND

Electricity flows from the Arduino, through the resistor, lights the LED, and returns to ground.

■ Quiz Time!

Circle the letter of the best answer for each question.

1. What is Arduino?

- A. A tiny computer that helps control lights, motors, and more
- B. A type of resistor
- C. A kind of fruit
- D. A video game console

2. What does Arduino let us make?

- A. Only boring things
- B. Cool projects with electronics and coding
- C. Sandwiches
- D. Paper airplanes

3. What does LED stand for?

- A. Light Emitting Diode
- B. Light Energy Device
- C. Long Electric Diode
- D. Light Electric Detector

4. An LED glows when...

- A. It gets cold
- B. Electricity passes through it
- C. It gets wet
- D. It is shaken

5. Which of these is NOT a reason to use external LEDs?

- A. Brighter light
- B. Different colors available
- C. Can be placed anywhere in a project
- D. They never need any power

6. What does a resistor do in a circuit?

- A. Makes the LED brighter forever
- B. Controls the amount of electricity flowing
- C. Stores electricity forever
- D. Creates new electricity

7. What can happen to an LED WITHOUT a resistor?

- A. It becomes cooler
- B. It works perfectly forever
- C. It might burn out
- D. Nothing happens at all

8. What happens to an LED WITH a resistor?

- A. It never lights up
- B. It stays safe and glows just right
- C. The Arduino stops working
- D. It turns off immediately

9. Which formula is used to calculate resistor value?

- A. $R = V_{\text{source}} \times V_{\text{LED}}$
- B. $R = (V_{\text{source}} - V_{\text{LED}}) / I_{\text{LED}}$
- C. $R = I_{\text{LED}} / V_{\text{source}}$
- D. $R = V_{\text{source}} + I_{\text{LED}}$

10. In the example, what is V_{source} (the Arduino voltage)?

- A. 2V
- B. 5V
- C. 9V
- D. 12V

11. In the example, what is V_{LED} (the LED voltage)?

- A. 5V
- B. 3V
- C. 2V
- D. 1V

12. In the example, what is I_{LED} (the current)?

- A. 20 mA
- B. 50 mA
- C. 2 A
- D. 100 mA

13. What resistor value did we calculate in the example?

- A. 100 Ohms
- B. 150 Ohms
- C. 200 Ohms
- D. 50 Ohms

14. Which leg of the LED is the long leg (+)?

- A. The positive leg
- B. The negative leg
- C. The neutral leg
- D. The ground leg

15. Which leg of the LED connects to GND?

- A. The long leg
- B. The short leg
- C. The middle leg
- D. Both legs at once

16. What should you always do before powering on your circuit?

- A. Turn off all the lights
- B. Double-check your connections
- C. Remove the resistor
- D. Disconnect the Arduino

17. In the simple circuit diagram, what comes right after Arduino Pin 13?

- A. The LED
- B. GND
- C. The resistor
- D. A battery

18. In the circuit, what happens after electricity passes through the resistor?

- A. It returns to the store
- B. It lights the LED
- C. It stops flowing
- D. It turns into water

19. Where does electricity go after it lights the LED?

- A. Back to Pin 13
- B. Into the resistor again
- C. To ground (GND)
- D. Nowhere — it disappears

20. Why do we need resistors in an LED circuit?

- A. To make the circuit look nicer only
- B. To keep the LED safe from too much electricity
- C. To make the Arduino turn on
- D. To change the LED's color

■ Answer Key

1. A

2. B

3. A

4. B

5. D

6. B

7. C

8. B

9. B

10. B

11. C

12. A

13. B

14. A

15. B

16. B

17. C

18. B

19. C

20. B

■ Great job learning about Arduino, LEDs, and resistors!

Keep Learning & Keep Building!