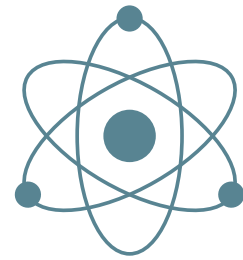


LIGHT UP THE ROOM

SERIES VS PARALLEL CIRCUITS

An Exciting Electricity Adventure





THE MYSTERY OF THE BROKEN LIGHTS


- Raju is ready for Diwali! But oh no, his fairy lights don't glow! 💡
- One tiny bulb is broken... and the **WHOLE** string went dark!
- Why do you think one broken bulb turned off the entire string?





ELECTRICITY IS A FLOWING DANCE!

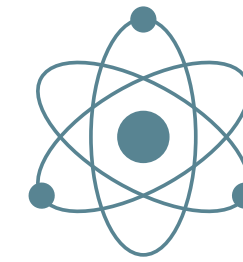Electricity flows like friends holding hands in a Garba circle! If one friend lets go, the dance stops. Electricity needs a complete, unbroken loop to light up bulbs!




WHAT HAPPENS WHEN THE LOOP BREAKS?

When Voltie runs in a complete loop, the bulb glows bright! But if one "hand" lets go and the loop breaks — Voltie stops and the light goes OFF!



SINGLE LANE ROADS: SERIES CIRCUITS

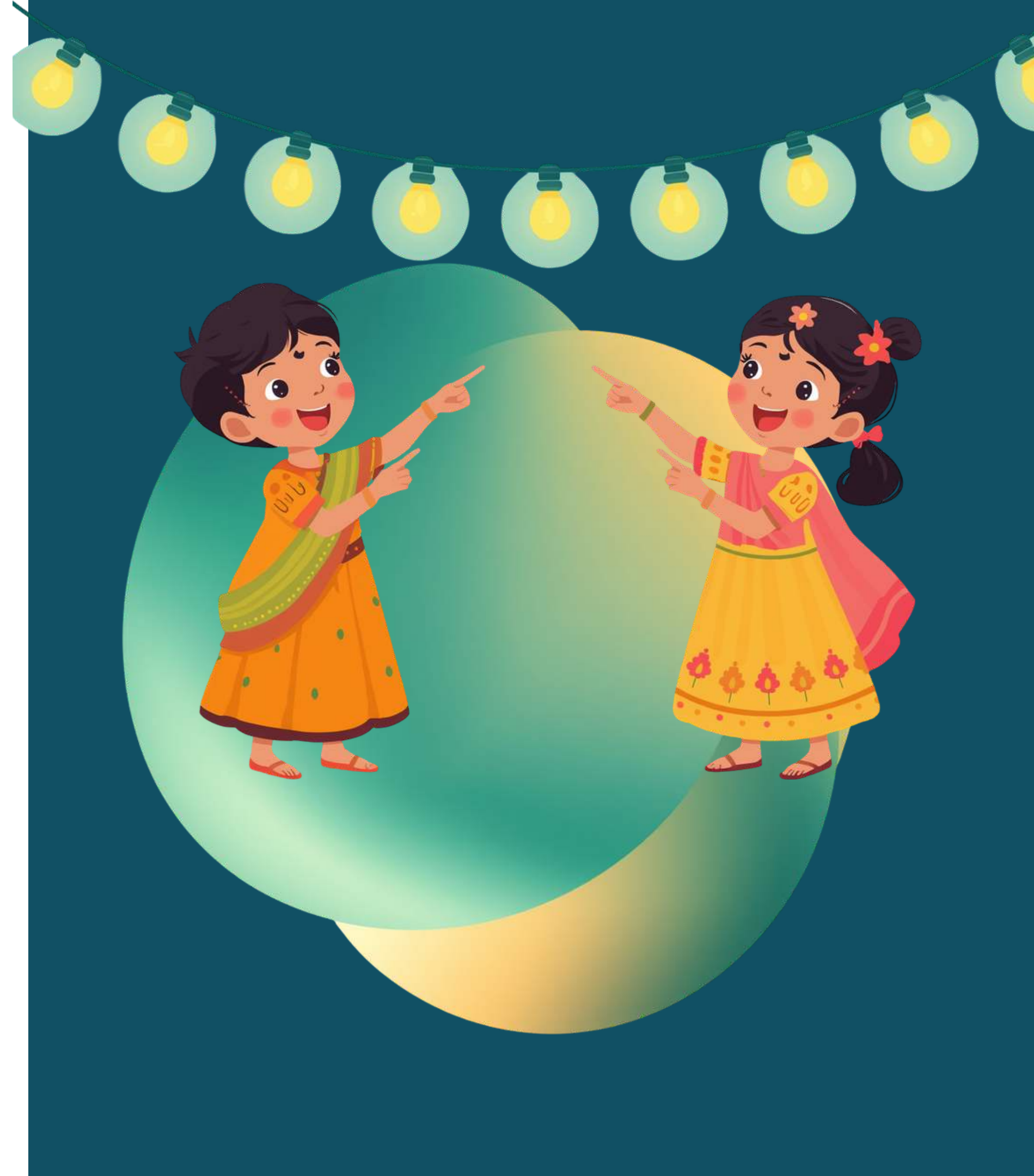Series circuits are like a single lane train
— all bulbs connected one after another.
If one bulb is removed, the whole train
stops moving!



PARALLEL CIRCUITS

Like multi-lane roads — each bulb has its own path! If one bulb turns off, the other still shines bright!



REAL-LIFE TREASURE HUNT!

Look at each item below!
Is it Series (single lane) or
Parallel (multi-lane)?



Diwali Jhallaar




Home Switchboard




Street Lights



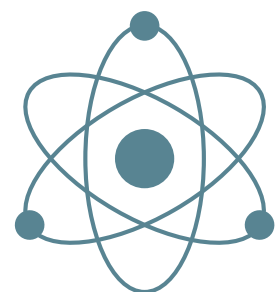

SERIES VS PARALLEL – QUICK COMPARISON!

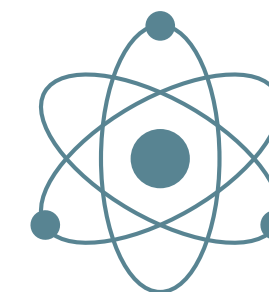

1


Series Circuit:
Single lane road —
one bulb off = ALL
bulbs go dark! 🚂

2

Parallel Circuit:
Multi-lane road —
bulbs work
independently! 🛣️


3

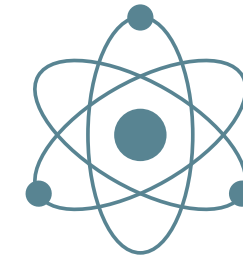**Remember: Train =
Series, Highway =
Parallel! 💡**




SAFETY PLEDGE!

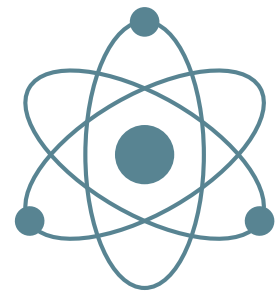**I will only explore circuits on
my screen or with toy
batteries. Never touch or try
real house plugs or sockets!**



RECAP: WHAT DID WE LEARN TODAY?

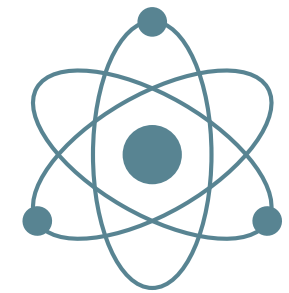

1

Electricity flows in a complete loop — like the Garba dance! 💡

2


Series circuits: one path — one bulb off means ALL go dark! (Diwali Jhallaar)

3

Parallel circuits: many paths — bulbs work independently! (Home switches)

MEET VOLTIE THE ELECTRON!

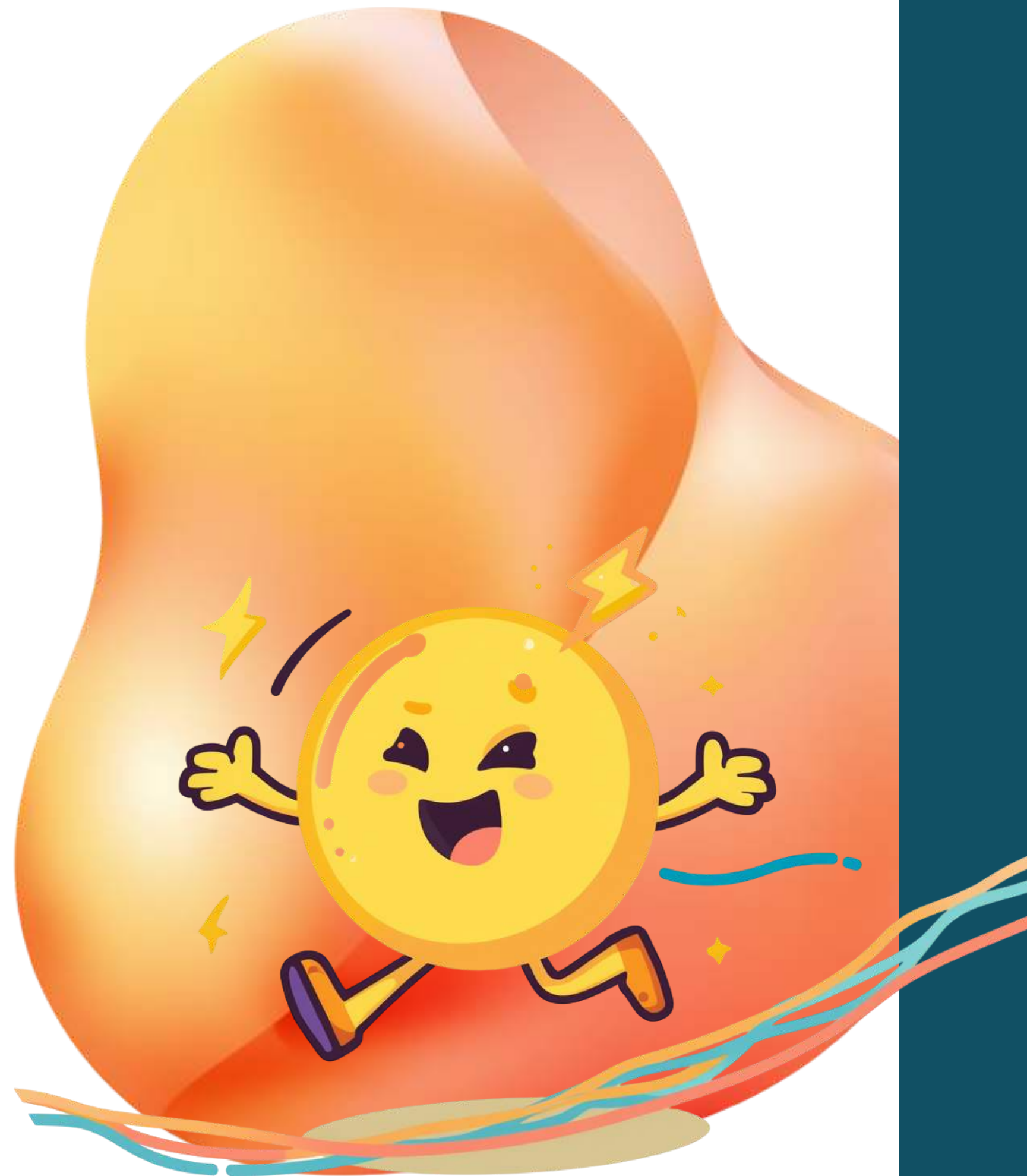Voltie loves to run fast and keep
your bulbs glowing bright!
Imagine electricity as tiny energy
friends zooming through wires —
that's Voltie and friends at work!





Final Poll: Test Your Circuit Smarts! ⚡

Q1: A string of fairy lights goes dark when one bulb breaks. Is this a Series or Parallel circuit?

Q2: You turn off one switch at home — do ALL appliances go off? Yes or No?



Thank You & Keep Exploring Safely!

You lit up your learning today! Remember: only explore
circuits on screen or with toy batteries. Never touch
real plugs or sockets! ⚡💥

