

LIGHT UP YOUR NAME!

SPARKLING INITIALS: MY FIRST PAPER CIRCUIT

Planrs Academy | Grade 1 Lesson Brief

THE SPARK HOOK

How does your name know it's time to shine? Look at the magical glowing nameplate and wonder!

Nabie

Imagine your own name sparkling like the stars in the night sky!

MEET THE COMPONENTS



Battery Power (Coin Cell)

The Power House of our circuit!



LED - The Little Lamp

Like a tiny traditional Diya that runs on magic power.



Copper Tape

The Magic Road for electricity to travel on.

THE NALA STORY

Electricity flows just like water in a "Nala" (pipe) or a small water channel.

If the pipe breaks, the water stops! Similarly, if the copper tape breaks, the light stops shining too.

The Two Friends: The battery has a Positive (+) and Negative (-) side. Both friends must be invited to the party for the lamp to light up!

Smooth Copper Road = Fast Electricity

LET'S BUILD! (PART 1)

Step 1

Write Your Initial: Draw your initial big and bold! Think of "A" for Arjun or "P" for Priya. Use the whole paper.

Step 2

Lay the Copper Road: Stick the copper tape smoothly around your letter. This is the magic path for your power.

LET'S BUILD! (PART 2)

Step 3

Place the Power House: Put the coin cell battery on the copper road to give it energy.

Step 4

Connect the Diya: Hold the LED gently like a tiny flower. Connect the legs to the copper ends.

Tip: LED legs must touch the copper tape properly—not loose or wobbly!



SHABAASH!

Your name is glowing like a star!
You did it, little inventor!

Science is everywhere around you. Keep exploring and
asking questions!